
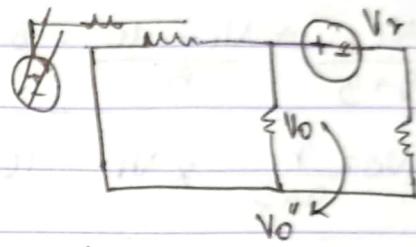
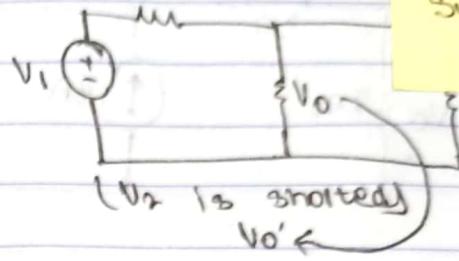



SUPERPOSITION PRINCIPLE

Slide 8
Superposition
Theorem

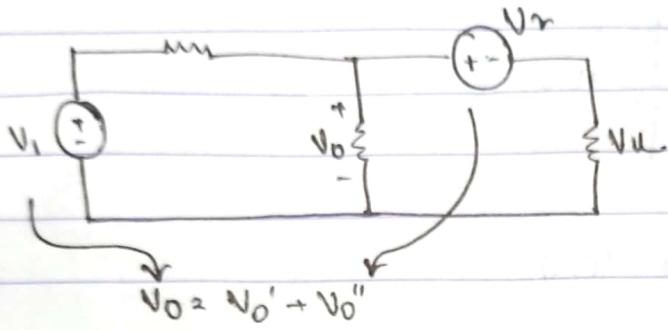

* Independent variables can be shorted.

* Dependent variables can't be shorted.

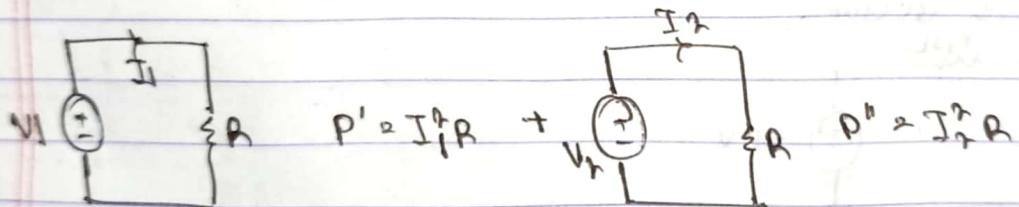


$$\textcircled{1} \quad P^2 R = I_1^2 R + I_2^2 R$$

$$(I_1 + I_2)^2 R + I_1^2 R + I_2^2 R$$

* Power is not a linear, so superposition is not valid

$$\frac{dV}{dI} = \frac{dV}{dI} = \frac{dV}{dI}$$

PROBLEM 1

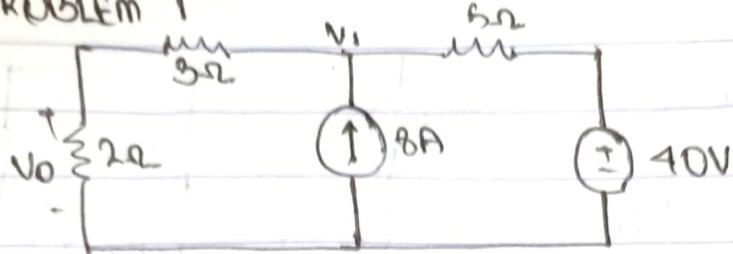


$$\frac{V_1}{2+3} + \frac{V_1 - 40}{3} = 8 \Rightarrow V_1 = 40V$$

$$V_o = \frac{2}{2+3} \times 40 = 16V$$


Superposition:-

40V source is active,

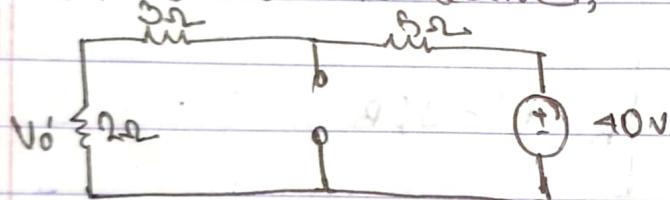

$$V_o' = \frac{2}{2+3+3} \times 40 = 8V$$

8A source is active

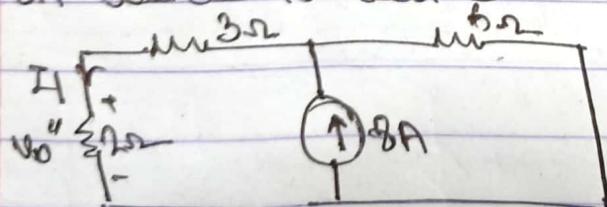

$$V_o'' = \frac{2}{2+3} \times 8 = 4V$$


$$V_o = V_o' + V_o''$$

$$V_o = 8 + 4 = 12V$$


According to the superposition principle,

$$\begin{aligned} V_o &= V_o' + V_o'' \\ &= 8 + 8 \\ &= 16V \end{aligned}$$

PROBLEM 7


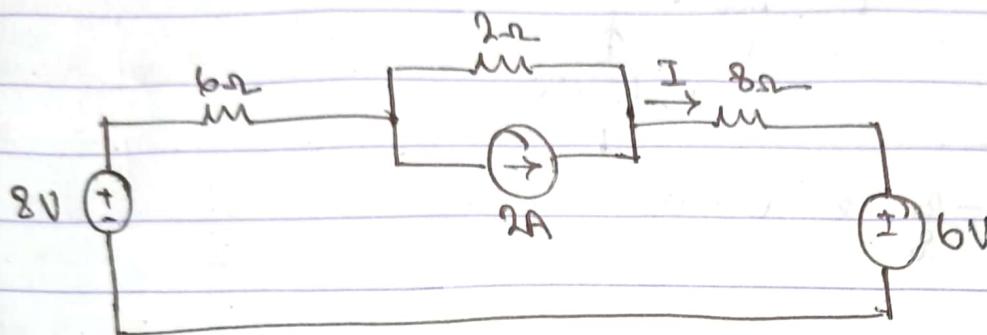


Only the 8V DC source is active

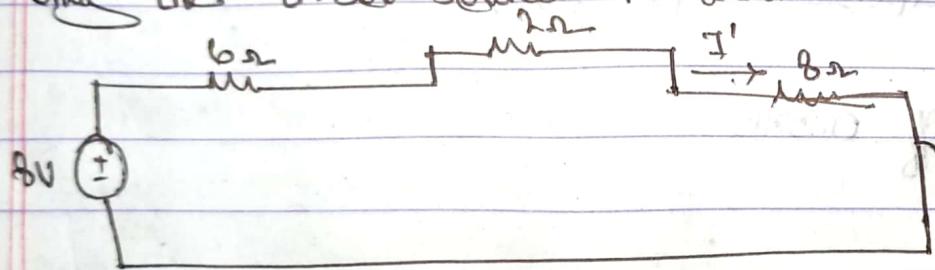


$$I' = \frac{8}{6+2+8} = 0.5A$$

Only the 2A source is active

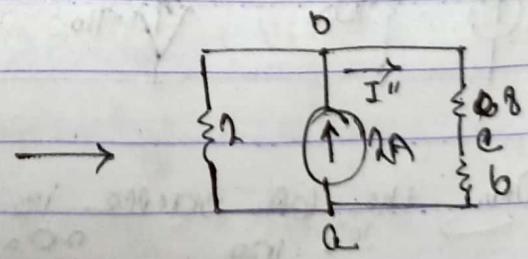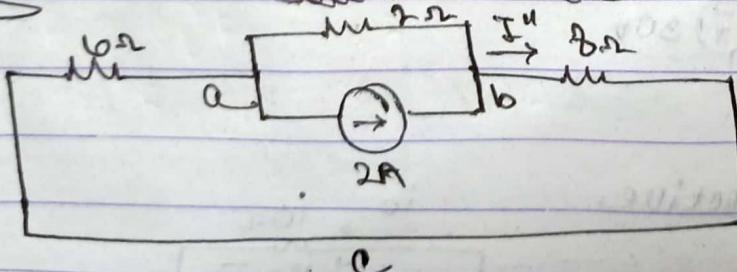

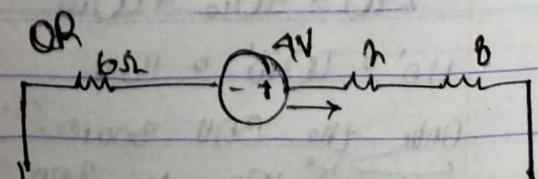
$$I'' = \frac{19}{(8+6)} \times 2 = 0.25A$$



$$I''' = \frac{4}{6+2+8} = 0.25A$$

Only the 6V source is active

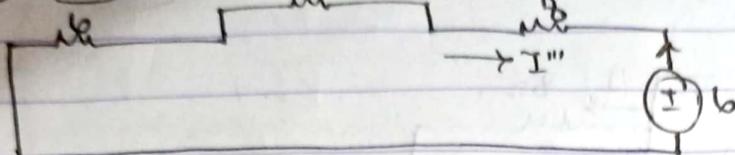

$$I'' = \frac{-6}{6+2+8} = \frac{-3}{16} = -0.375$$


According to the superposition principle,

$$I_0 = I' + I'' + I'''$$



$$= 0.6 + 0.26 - \frac{3}{16} = 0.375$$

$$= 0.375 \text{ A}$$

PROBLEM 4

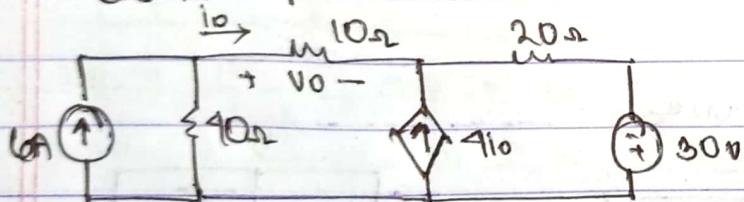


Only the 6A source is active

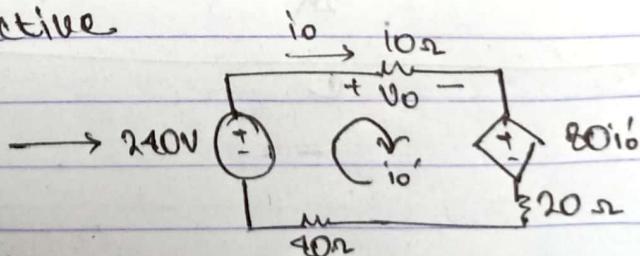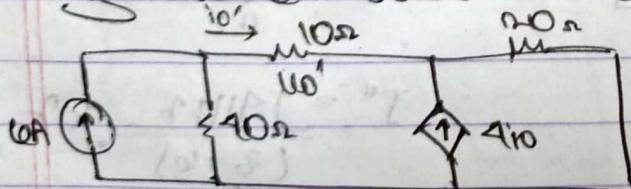

$$-240 + 40i_0' + 10i_0' + 80i_0' + 20i_0' = 0 \Rightarrow i_0' = 1.6 \text{ A}$$

$$V_0' = 10i_0' = 16 \text{ V}$$

Only the 30V source is active.

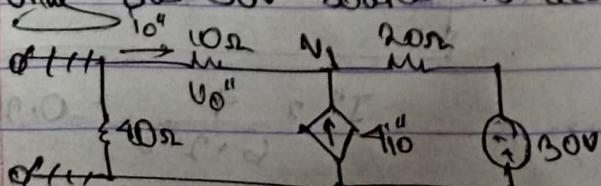

$$4i_0'' = \frac{V_1}{50} + \frac{V_1 + 30}{20} \quad [i_0'' = \frac{V_1}{50}]$$

$$\Rightarrow 4 \left(\frac{-V_1}{50} \right) = \frac{V_1}{50} + \frac{V_1 + 30}{20}$$

$$V_1 = 10 \text{ V}$$

$$i_0'' = \frac{(-10)}{50} = 0.2A$$

$$V_0'' = i_0'' \times 10 = 0.2 \times 10 = 2V$$


$$V_0 = V_0' + V_0''$$

$$= 16 + 2 = 18V$$


$$i_0 = i_0' + i_0''$$

$$= 1.6 + 1.2 = 1.8A$$

PROBLEM 6

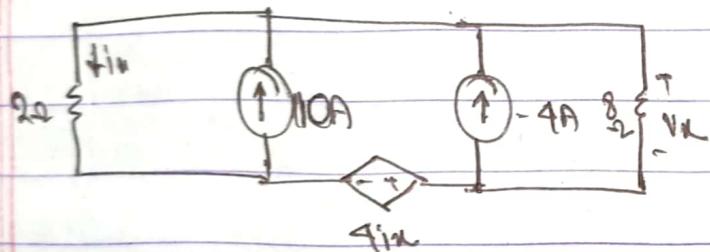

Only the 10A source is active

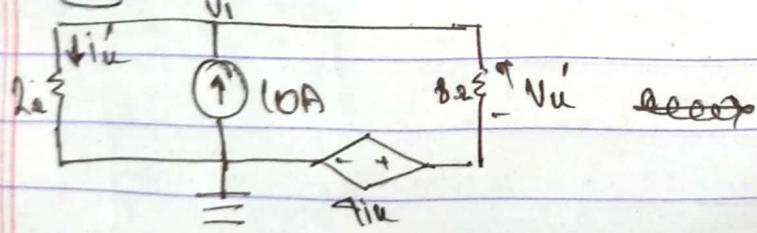


$$10 = \frac{V_1}{2} + V_1 - 4i_{in}' \quad [i_{in}' = \frac{V_1}{2}]$$

$$80 = 6V_1 - 4\left(\frac{V_1}{2}\right) \quad [i_{in}' = \frac{80}{3}]$$

$$V_1 = \frac{80}{3} = 26.67V \quad [i_{in}' = \frac{40}{3}]$$

$$V_L' = V_1 - 4i_{in}' \times 8 = \frac{80}{3} - 4\left(\frac{40}{3}\right) \times 8 = -\frac{80}{3}V$$

Only the -4A source is active

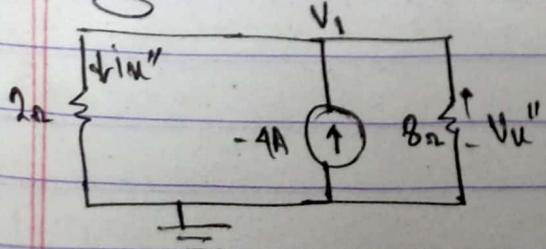

$$i_{in}'' = \frac{V_1 - 0}{2}$$

$$-4 = \frac{V_1}{2} + \frac{V_1 - 4i_{in}''}{8}$$

$$-4 = \frac{V_1}{2} + \frac{V_1 - \frac{V_1}{2}}{8}$$

$$\not\Rightarrow -32 = 6V_1 - 2V_1$$

$$V_1 = -\frac{32}{5}V$$

$$\frac{V_1 - V_{u''}}{8} \times 8 = V_{u''}$$


$$V_{u''} = 32 \text{ V}$$

$$\text{Acc } V_{u''} = V_{u'} + V_{u''} = -\frac{80}{3} + \frac{32}{3} = -16 \text{ V}$$

$$V_S = 0 \text{ V} \Rightarrow 0$$

$$V_{u'} = 0$$

$$A_{u''} = 8$$

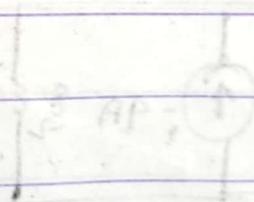

$$R_{u''}$$

$$V_{u''}$$

$$A_{u''}$$

$$R_u'$$

$$V_{u'}$$

$$A_u'$$

$$R_u''$$

$$V_{u''}$$

$$A_u''$$

$$R_u'''$$

$$V_{u''}$$

$$A_u'''$$

$$R_u''''$$

$$V_{u''}$$

$$A_u''''$$

$$R_u'''''$$

$$V_{u''}$$

$$A_u'''''$$

$$R_u''''''$$

$$V_{u''}$$

$$A_u''''''$$

$$R_u'''''''$$

$$V_{u''}$$

$$A_u'''''''$$

$$R_u''''''''$$

$$V_{u''}$$

$$A_u''''''''$$



WEDNESDAY

DATE: 17/11/22


THEVENIN'S THEOREM & NORTON'S THEOREM

Slide 9
Thevenin's and
Norton's Theorem



THEVENIN'S THEOREM

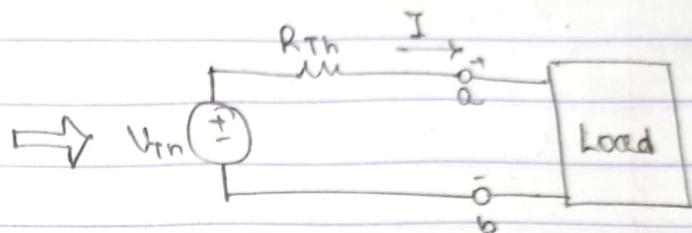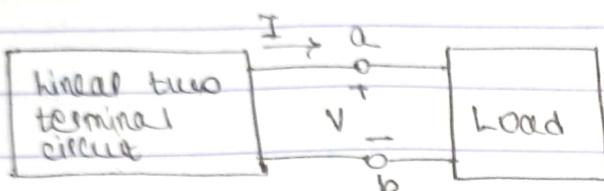

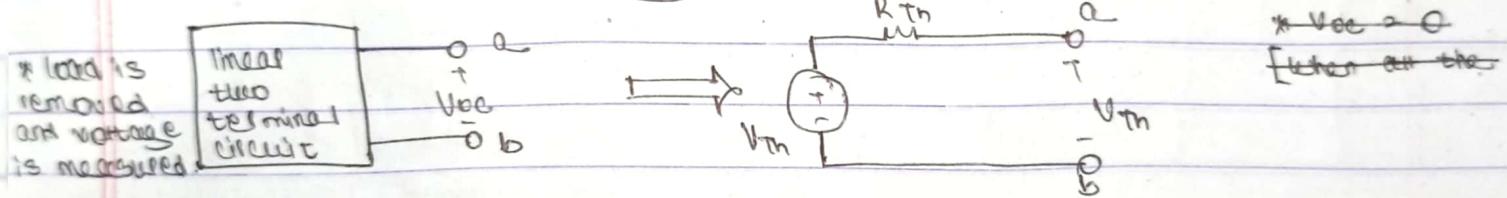To check whether the original circuit & Thevenin equivalent circuit:—




(1) $V_{oc} = V_{th}$

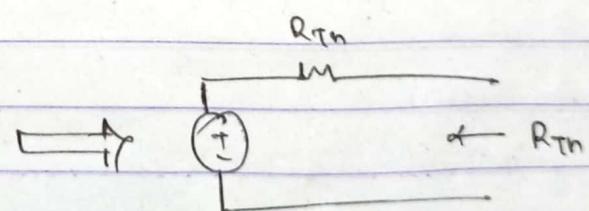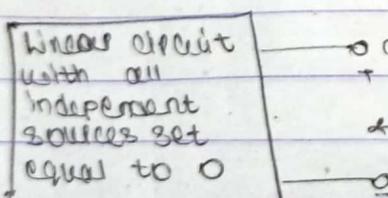

(2) $R_{eq} = R_{th}$


(3) $I_{sc} = \frac{V_{th}}{R_{th}}$

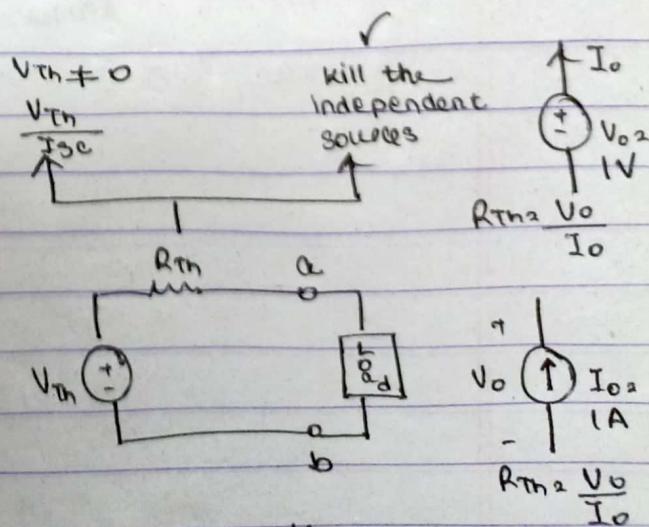


* $V_{oc} = 0$
 $I_{sc} = 0$
 $R_{th} = \frac{0}{0}$ is undetermined

special case

Problem 1

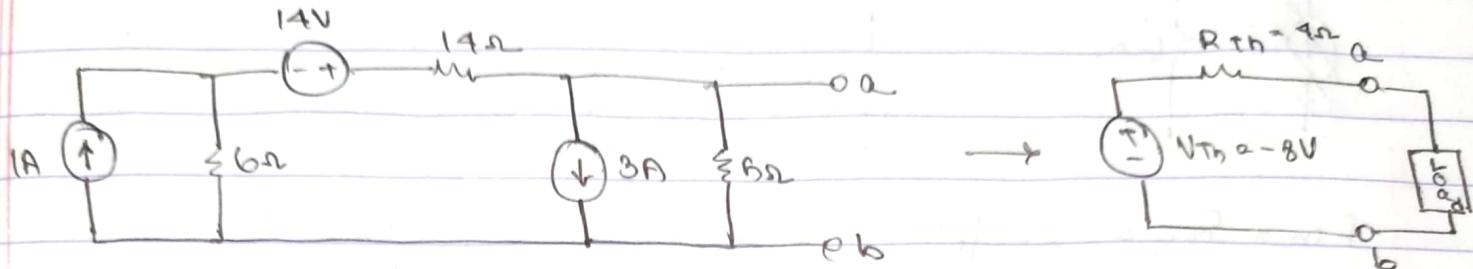

31st 8T

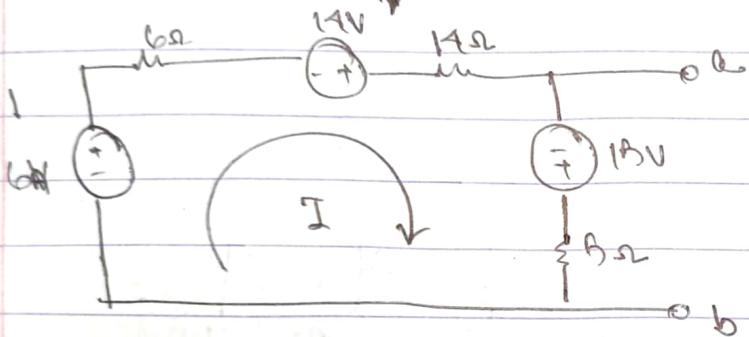


$$-6 + 6I - 14 + 14I - 18 + 5I = 0$$

$$I^2 \frac{4}{5} = 1.4A$$

$$-V_{Th} - B + BI = 0$$

$$N_{Th} = 8 N$$

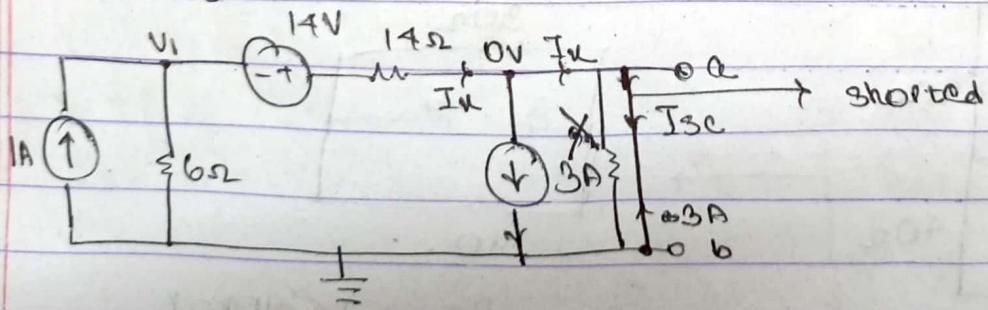


$$I_2 \frac{V_1}{6} + V_1 - \frac{1-14}{14} = 0 \Rightarrow V_1 = 0 \text{ V}$$

$$I_{AB} = \frac{V_1 - (-1A)}{1A} = 0 \quad \Rightarrow \quad \frac{0 + 1A}{1A} = 1A \quad [V_1 = 0]$$

$$T_{30} = T_{10} \bar{+} 3 = 1 - 3 = -2A$$


$$R_{Th} = \frac{V_{Th}}{I_{Th}} = \frac{8}{2} = 4 \Omega$$

method-2

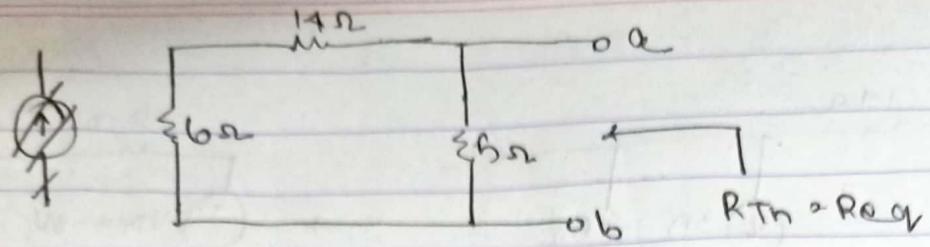

$$R_{Th} = R_{eq} = 20 \parallel 3 = \left(\frac{1}{20} + \frac{1}{3} \right)^{-1} = 1 \Omega$$


Problem 2

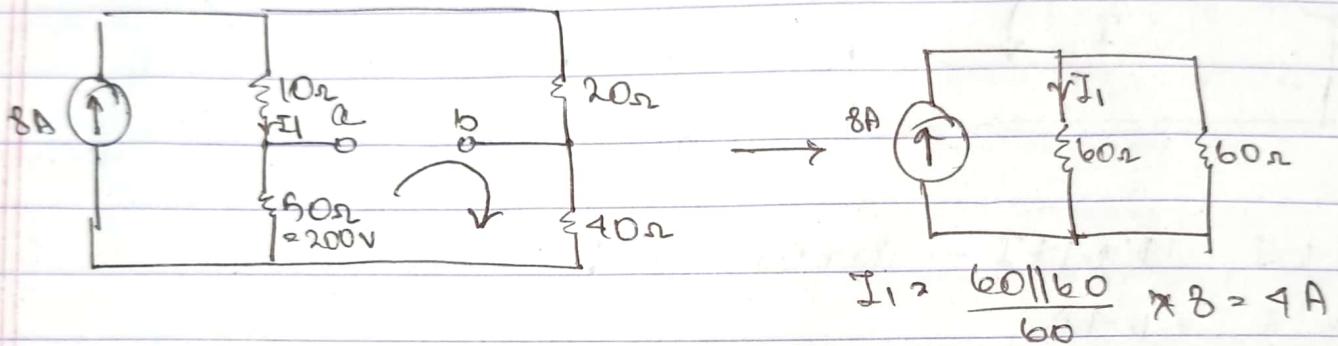

$$I_1 = \frac{60 \parallel 60}{60} \times 8 = 4A$$


$$-200 + V_{Th} + 160 = 0$$

$$V_{Th} = 40V$$

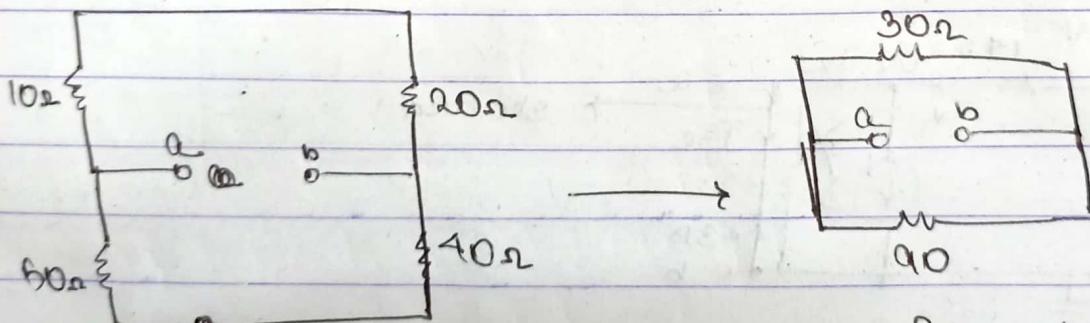

$$R_{ab} = R_{Th} = [30 \parallel 90] \\ = \left(\frac{1}{30} + \frac{1}{90} \right)^{-1} \\ = 22.5 \Omega$$

Problem 7

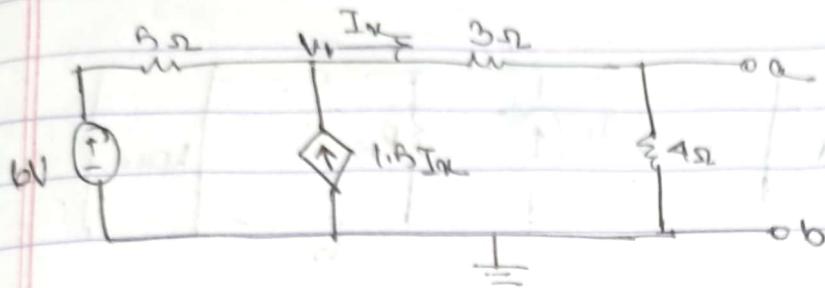


$$\frac{V_1 - 6}{5} + \frac{V_1}{3} = 1.5I_R \quad [I_R = \frac{V_1}{3}]$$

$$\frac{V_1 - 6}{5} + \frac{V_1}{3} = 1.5 \left(\frac{V_1}{3} \right)$$

$$V_1 = \frac{28}{3} \quad V = 9.33V$$
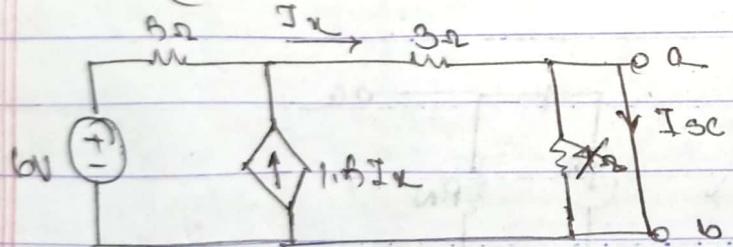
$$V_m = \left(\frac{V_1}{3} \right) \times 4 = 5.33V$$



$$I_2 = I_{sc}$$

$$-6 + 5I_1 + 3I_2 = 0 \quad \text{--- (1)}$$

$$I_2 - I_1 = 1.5I_R$$


$$I_2 - I_1 = 1.5I_2$$

$$-I_1 - 0.5I_2 = 0 \quad \text{--- (2)}$$

$$I_1 = -6A, I_2 = 12A$$

$$I_{sc} = 12A$$
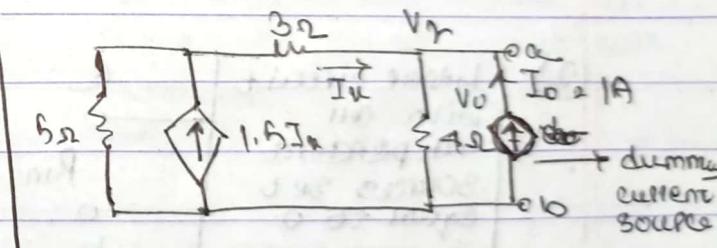
$$\textcircled{a} \quad R_m = \frac{V_m}{I_{sc}} = \frac{5.33}{12} = \frac{1}{9} \Omega$$



$$V_0 = V_m$$

OR KCL at V_1,

$$1.5I_R = \frac{V_L}{5} + \frac{V_1 - V_m}{3}$$

$$1.5 \left(\frac{V_1 - V_m}{3} \right) = \frac{V_L}{5} + \frac{V_1 - V_m}{3} \quad [I_R = \frac{V_1 - V_m}{3}]$$

KCL at V_m

$$I_2 \frac{V_m - V_1}{3} + \frac{V_m}{4}$$

$$V_1 = V_m = V_{m0}$$

$$R_m = \frac{V_m}{I_0} =$$


LECTURE

15


MONDAY

DATE: 21/11/22


NORTON'S THEOREM

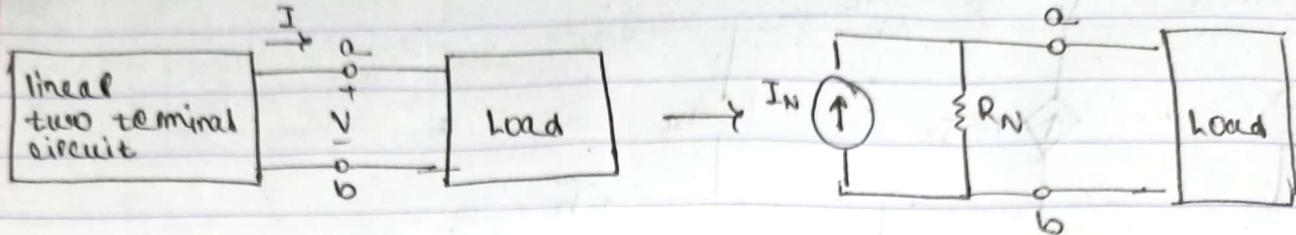

Original circuit

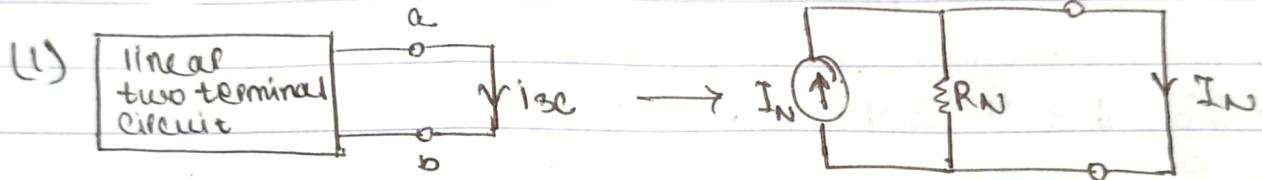


$$I_{sc} = I_N$$

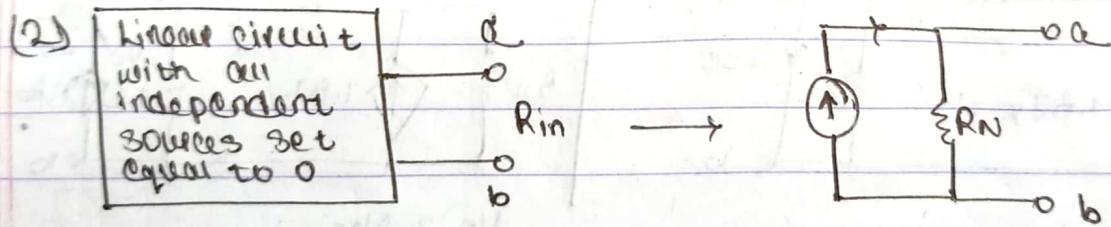


$$R_{in} = R_N$$

$$(3) V_{oc} = I_N R_N$$




Thevenin \leftrightarrow Norton

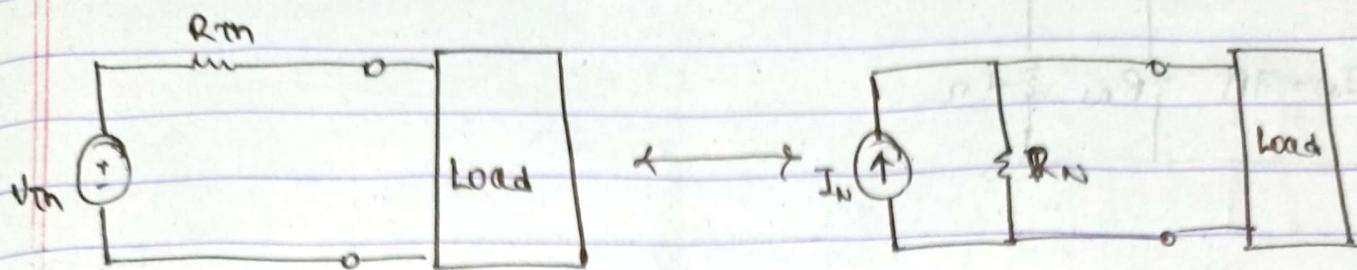


Problem 7

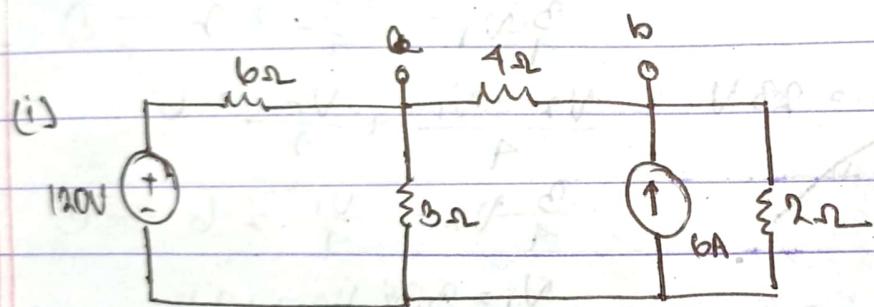

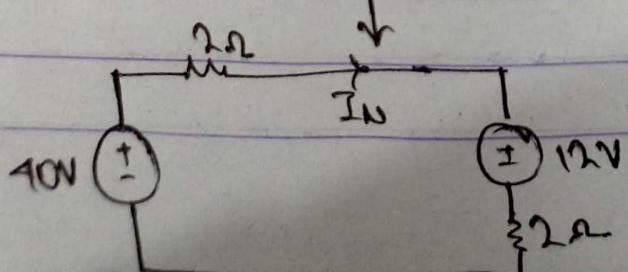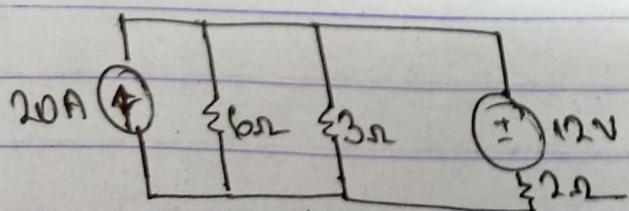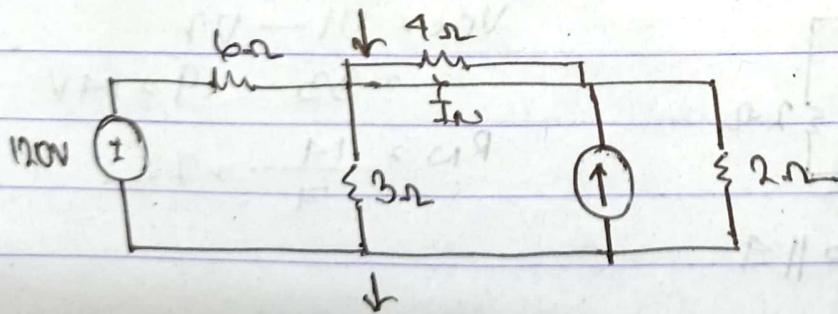
* The components which are connected to the terminals mentioned in question - are the all load


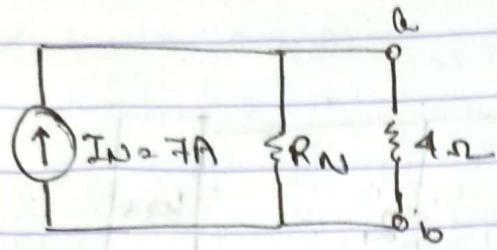
$$I_N = \frac{40 - 12}{2} = 14 \text{ A}$$


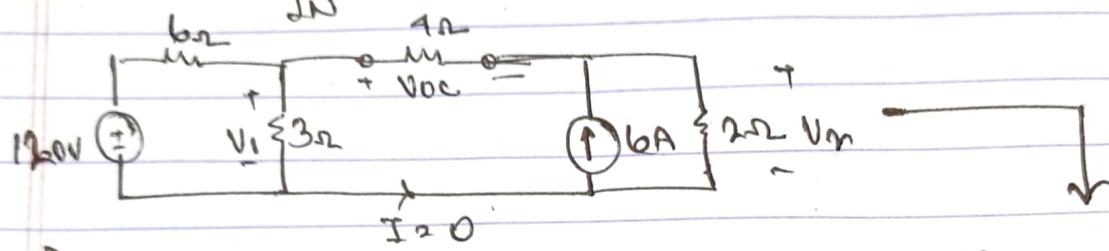
$$\text{method-1 (i)} \quad R_N = \frac{V_{OC}}{I_N}$$



~~$$V_2 = \frac{3}{3+6} \times 120 = 40 \text{ V}$$~~

~~$$V_2 = 6 \times 2 = 12 \text{ V}$$~~

~~$$V_{OC} = V_1 - V_2 = 40 - 12 = 28 \text{ V}$$~~

~~$$R_N = \frac{V_{OC}}{I_N} = \frac{28}{7} = 4 \Omega$$~~

$$\frac{V_1 - 120}{3} + \frac{V_1}{4} + \frac{V_1 - V_2}{4} = 0$$

$$\frac{3}{4}V_1 - \frac{V_2}{4} = 7 \quad \text{--- (i)}$$

$$\frac{V_2 - V_1}{4} + \frac{V_2}{2} = 6$$


$$\frac{3}{4}V_2 - \frac{V_1}{4} = 6 \quad \text{--- (ii)}$$

$$V_1 = 33 \text{ V}, V_2 = 19 \text{ V}$$

$$V_{OC} = V_1 - V_2$$

$$= 33 - 19 = 14 \text{ V}$$

$$R_N = \frac{14}{7} = 2 \Omega$$

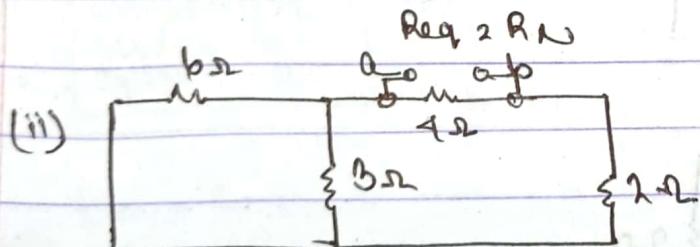

$$R_{eq} = ((6||3) + 2) = R_N \parallel 4$$

$$= (2 + 2) \parallel 4$$

$$R_N = 1 \parallel 1 = 1$$

$$R_N = 2 \Omega$$

$$V_{OC}$$

$$V_1$$





$$V_2$$

$$V_{OC}$$




$$V_1$$

$$V_2$$

Problem 8

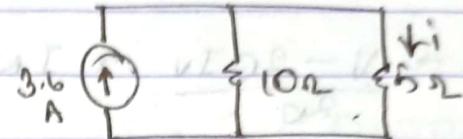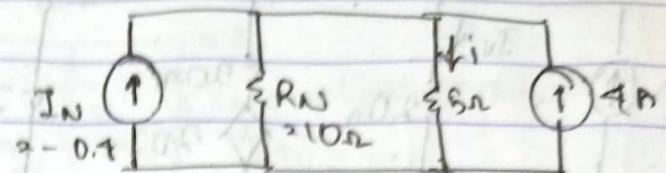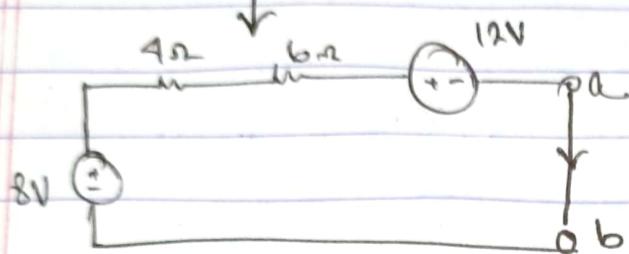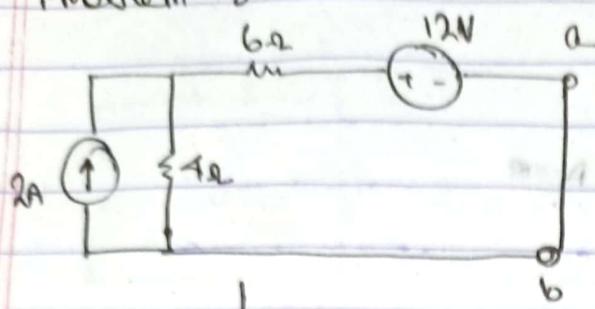
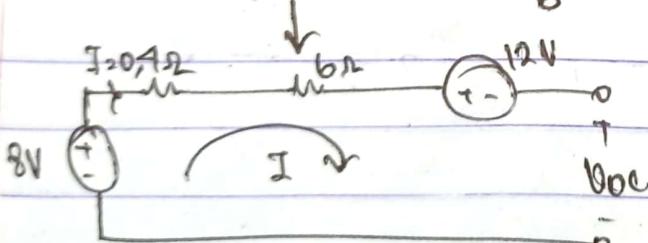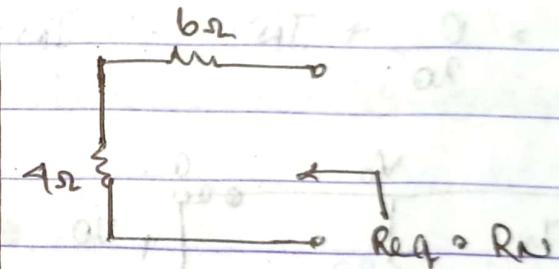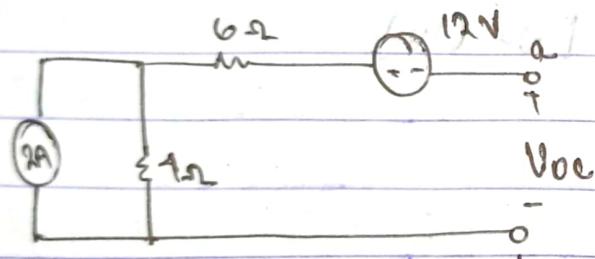
$$I_{IN} = \frac{8 - 12}{4 + 6} = -0.4 \text{ A}$$



$$-8 + 4I + 6I + 12 = V_{OC} = 0$$

$$V_{OC} = -4$$

$$R_N = \frac{V_{OC}}{I_{IN}} = \frac{-4}{-0.4} = 10 \Omega$$


OR

$$I = \frac{V_{OC}}{R_N + R_{IN}} = \frac{-4}{10 + 10} = -0.2 \text{ A}$$

$$I = \frac{V_{OC}}{R_N} = \frac{-4}{10} = -0.4 \text{ A}$$

$$V_{OC} = I R_N$$

Problem 10

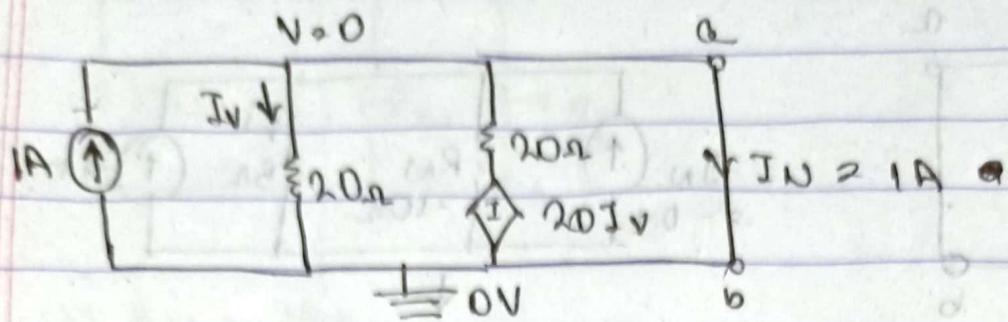


$$1 = \frac{V}{20} + \frac{V - 20I_v}{20} + I_N$$

$$\Rightarrow 1 = \frac{V}{20} + V - 20\left(\frac{V}{20}\right) + I_N$$

$$\Rightarrow 1 = \frac{V}{20} + I_N$$
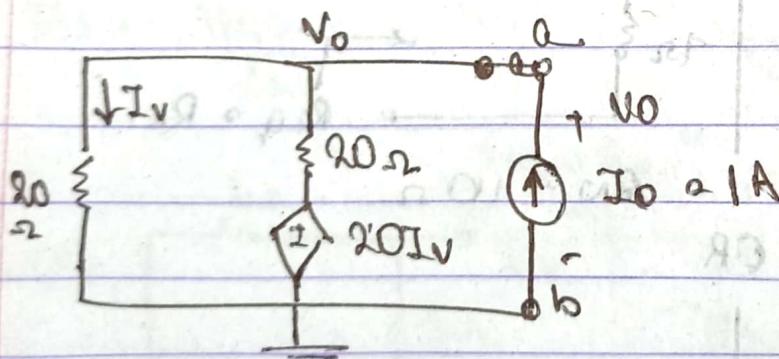
$$\Rightarrow 1 = \frac{0}{20} + I_N \quad \therefore I_N = 1A \quad [V_o = 0V]$$




$$\frac{V_o}{20} + V_o - 20 = 20I_v = 1$$

$$\frac{V_o}{20} + V_o - 20\left(\frac{V_o}{20}\right) = 1$$

$$V_o = 20V$$

$$R_N = \frac{V_o}{I_o} = \frac{20}{1} = 20\Omega$$

Problem 11

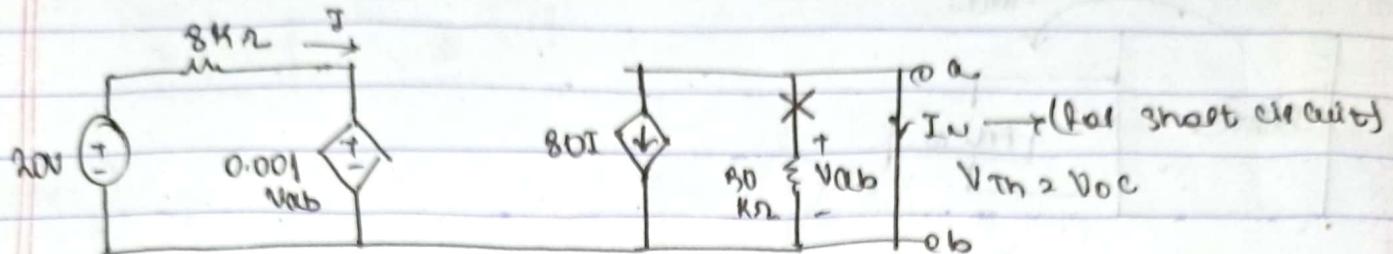

$$V_{ab} = V_{Th} = -80I \times 80$$

$$2 = 1000 I$$

$$2 = 4000 \left(2 - \frac{0.001 V_{ab}}{8} \right)$$


$$V_{ab} = -2000 \text{ V}$$

$$I_N = -80I = -80 \left(2 - \frac{0.001(-2000)}{8} \right) = -22.025 \text{ mA} = -20 \text{ mA}$$

$$R_N = \frac{V_{oc}}{I_N} = \frac{2 - 2000}{20} = 1000 \text{ k}\Omega$$


WEDNESDAY

MAXIMUM POWER TRANSFER THEOREM

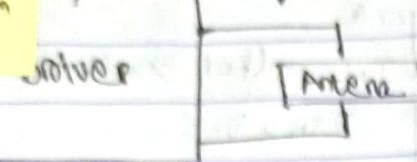Slide 10
Maximum Power Transfer TheoremP_{max}

$$\eta^2 \frac{P_{out}}{P_{in}} * 100\%$$

$$R_m = 1.99 \text{ k}\Omega$$

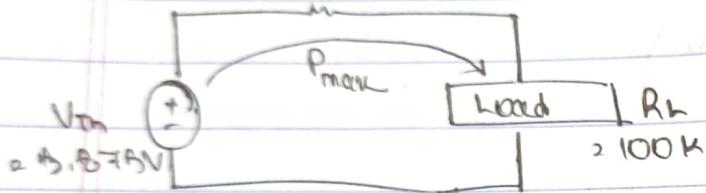

QAK 108 - 4.11.2023

LOAD = 5

$$P = I^2 R = \frac{V^2}{R} = VI$$



$$I = \frac{V_m}{R_m + R_L} = 0.058 \text{ mA}$$

$$1.99 + 100$$

$$P_{out} = I^2 R = 0.333 \text{ mW}$$

$$P_{in} = 5.875 \times 0.058 \approx 0.34 \text{ mW}$$
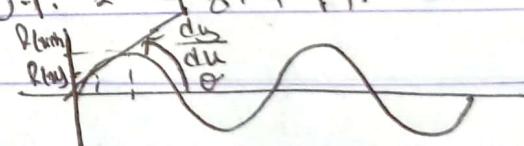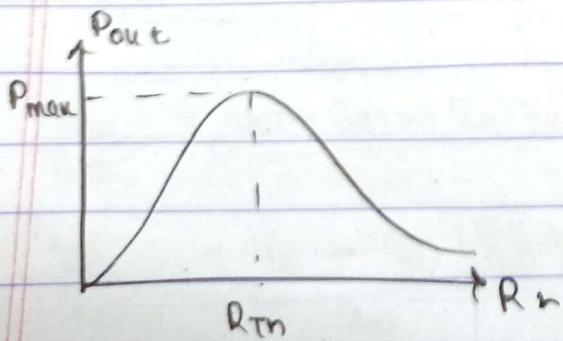
$$\eta^2 \frac{P_{out}}{P_{in}} * 100\% = \frac{0.333}{0.34} * 100\% = 98.54\%$$



$$\frac{dy}{dx} = \lim_{\Delta x \rightarrow 0} \frac{\Delta y}{\Delta x}$$

$$\frac{dy}{dx} = \lim_{h \rightarrow 0} \frac{f(x+h) - f(x)}{h}$$

$$\frac{dy}{dx} = \tan \theta, \frac{dy}{dx} = 0$$




$$P_{out} = I^2 R = \left(\frac{V_m}{R_m + R_L} \right)^2 R_L = \frac{V_m^2 R_L}{(R_m + R_L)^2}$$

$$\frac{dp}{dr_L} = 0 \rightarrow R_L \text{ at max}$$

$$P_{max} = \frac{V_m^2}{(2R_m)^2} R_m \quad [R_L = R_m]$$

$$P_{max} = \frac{V_m^2}{4R_m}$$

Problem 1

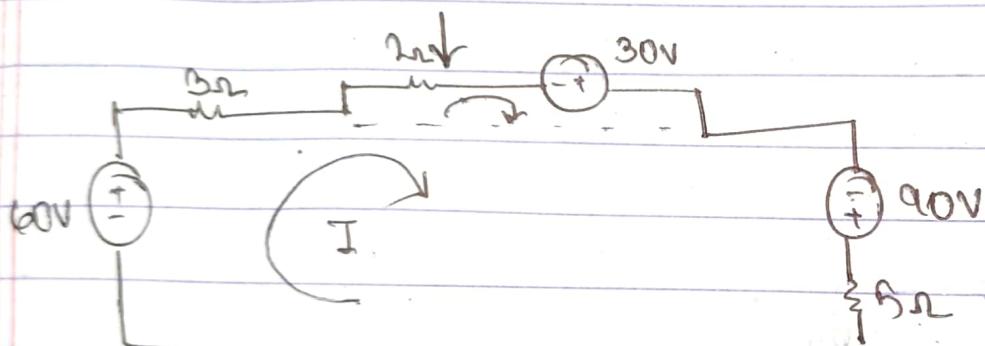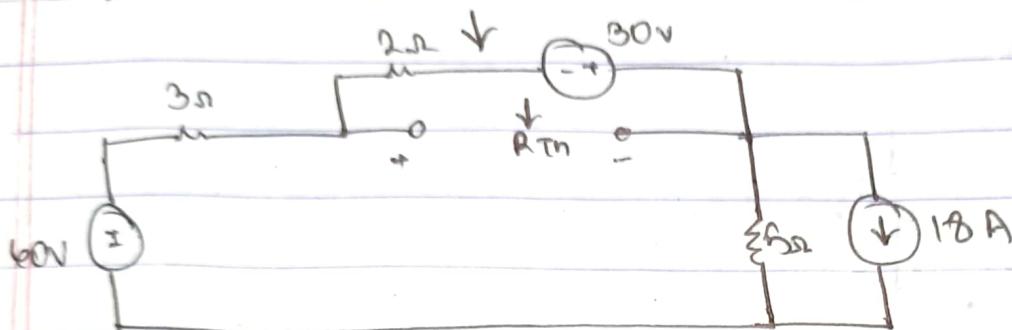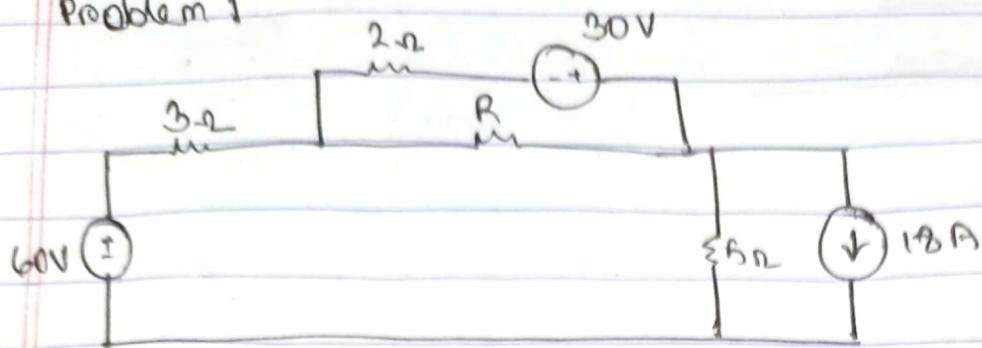


$$-60 + 3I + 2I - 30 - 90 + 5I = 0$$

$$\textcircled{1} \quad I = 18 \text{ A}$$

$$-V_{Th} + 2I - 30 = 0$$

$$\Rightarrow V_{Th} = 6 \text{ V}$$

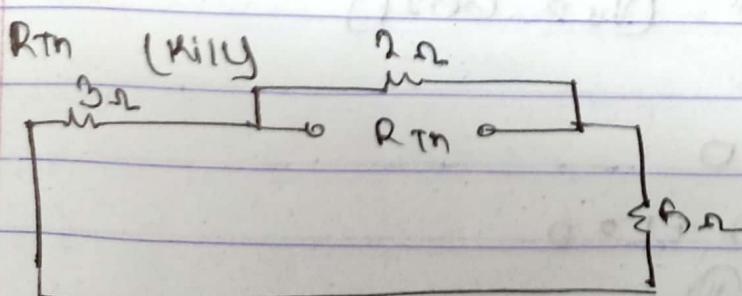


$$R_{Th} = (3 + 5) \parallel 2$$




$$R_{Th} = 1.6 \Omega$$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = 5.625 \text{ W}$$

$$R = \frac{P_{RL}}{P_{RL} + P_{Th}} = \frac{\frac{P_{in}}{r}}{\frac{P_{in}}{r} + P_{Th}} = 0.1 \text{ V}$$

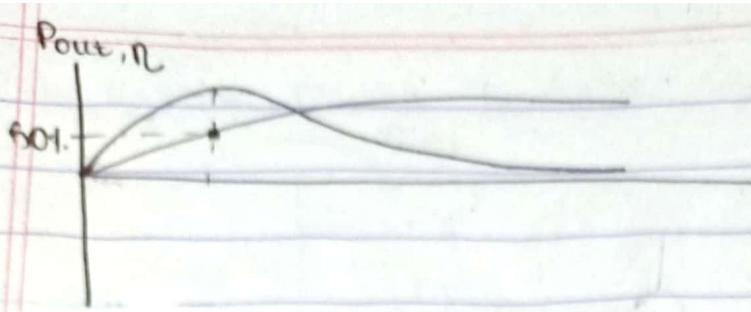

Problem 3

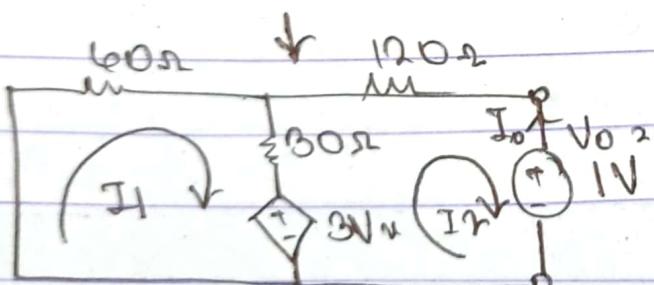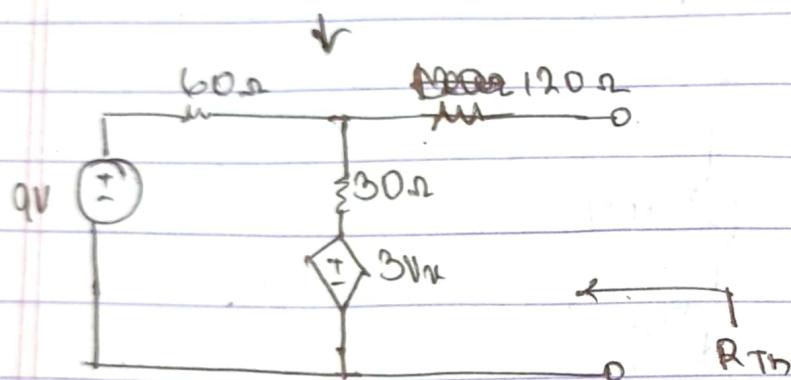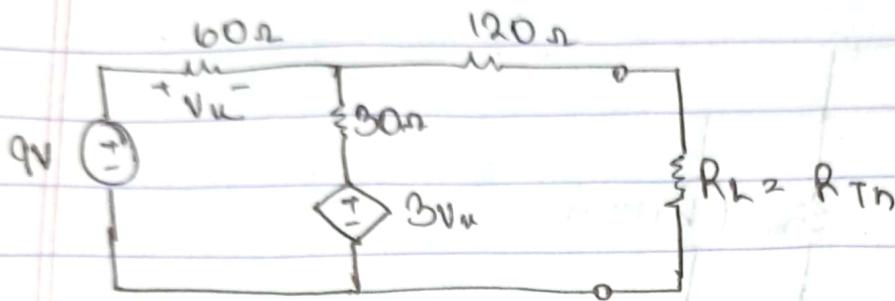

$$60I_1 + 30(I_1 - I_2) + 3V_u = 0 \quad (V_u = 60I_1)$$

$$180I_1 - 30I_2 = 0 \quad \text{--- (1)}$$

$$-3V_u + 30(I_2 - I_1) + 120I_2 + 1 = 0$$

$$-3(60I_1) + 30(I_2 - I_1) + 120I_2 + 1 = 0$$


$$-210I_1 + 150I_2 = -1 \quad \text{--- (2)}$$

$$I_2 = 7.89 \times 10^3 \text{ A}$$

$$I_0 = I_2 = 7.89 \times 10^3 \text{ A}$$

$$R_{Tn} = \frac{V_o}{I_0} = \frac{1}{7.89 \times 10^3} = 126.7 \text{ ohms}$$

P_{max} = 4

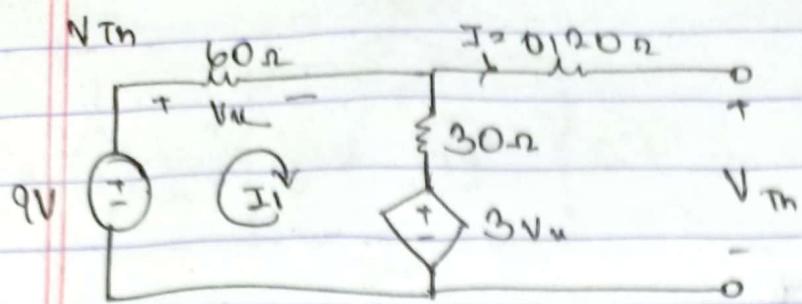

$$-9 + 60I_1 + 30I_1 + 3V_u = 0 \quad V_u = 60I_1$$

$$-9 + 60I_1 + 30I_1 + 3(60I_1) = 0 \Rightarrow 0$$

$$I_1 = 0.0333 \text{ A}$$

$$V_{Th} = 30 \times 0.0333 + 30I_1 + 3V_u$$

$$= 30(0.0333) + 3(60 \times 0.0333)$$

$$= 6.993 \text{ V}$$




$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(6.993)^2}{4(126.7)} \times 100 = 0.0963 \text{ W}$$

$$I_{Th} = \frac{V_{Th}}{R_{Th}}$$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

$$= \frac{I_{Th}^2 R_{Th}}{4} = \frac{I_{Th}^2 R_{Th}}{4} = \frac{I_{Th}^2 R_N}{4}$$

Problem 5

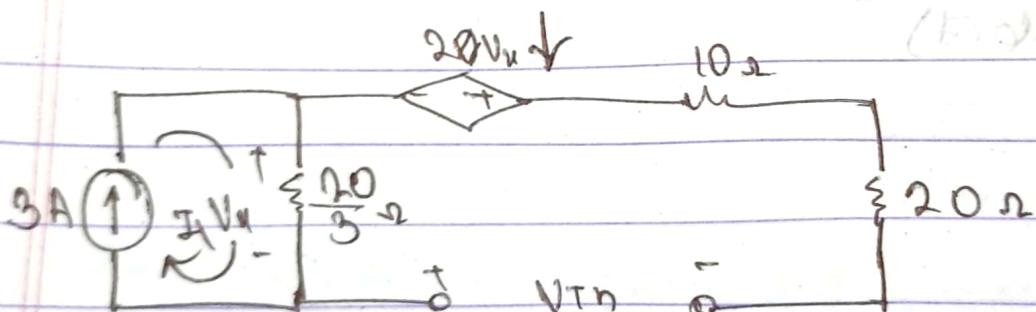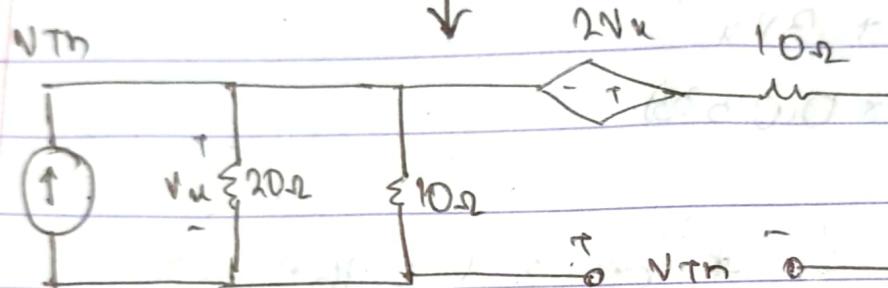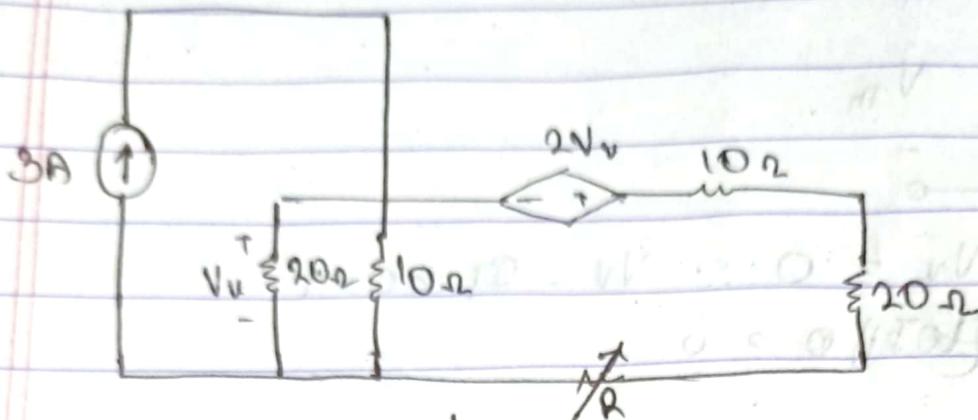


$$Vn = 20 \text{ V}$$

$$Vn = \frac{20}{3} \text{ (3)} = 20 \text{ V}$$

KVL at loop 2

$$-Vn - 2Nv + 0 + 0 - Vn = 0$$

$$Vn = -60 \text{ V}$$

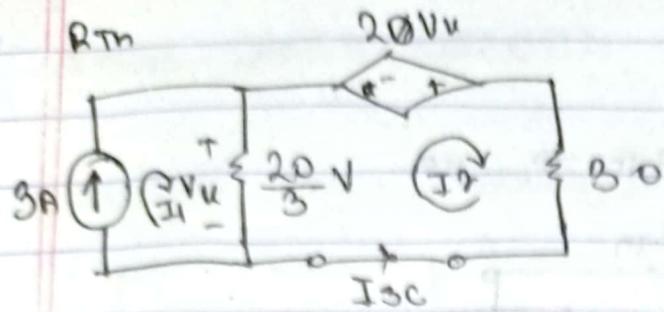

$$II = 3A$$

KNL at loop 2

$$\frac{20}{3}(I_2 - I_1) - 20u + 30I_2 = 0 \quad [u = (I_1 - I_2)\left(\frac{20}{3}\right)]$$

$$\frac{80}{3}(I_2 - I_1) - 2 \left[(I_1 - I_2) \left(\frac{20}{3} \right) \right] + 30I_2 = 0$$

$$\frac{20}{3} (I_2 - 3) - 2 \left[(3 - I_2) \left(\frac{20}{3} \right) \right] + 30 I_2 = 0$$

$$I_B = 1.2 \text{ A}$$

$$I_{3c^2} - I_{f^2} = 1.2 \text{ A}$$


$$R_{Th} = \frac{V_{Th}}{I_{Th}} = \frac{-60}{-12} = 50 \Omega$$

$$P_{max} = \frac{V^2 R}{4R_{Th}} = \frac{(-60)^2}{4(60)} = 18 \text{ W}$$


MONDAY

FIRST ORDER CIRCUITS

Power (Load)

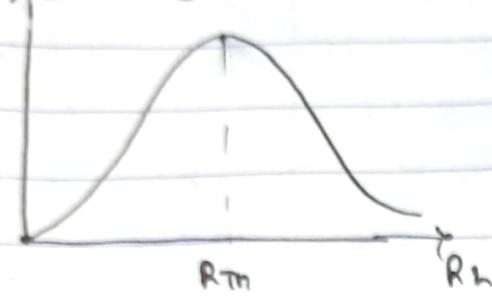

$$R_N \rightarrow R_m \rightarrow -V_e$$

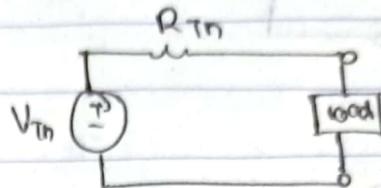

$$\frac{dP}{dR_L} = 0$$

Maxima \leftarrow \downarrow Minima

$$R_L = R_m$$

* When load supplies to R_m instead of voltage source, then R_m comes in $-ve$.