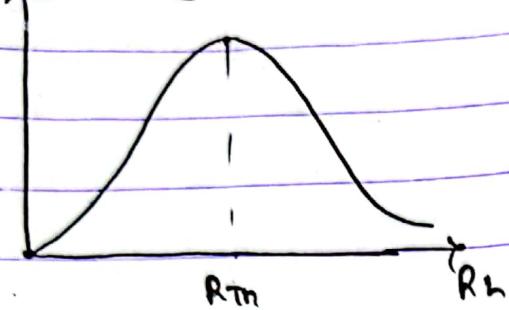



MONDAY

FIRST ORDER CIRCUITS

Power (Load)


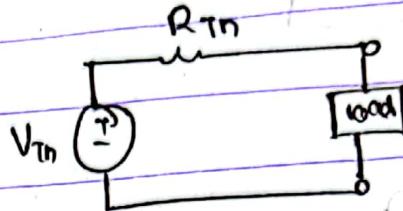
$$P_N \rightarrow R_{Th} \rightarrow -V_o$$



$$\frac{dP}{dR_L} = 0$$


Maxima \leftarrow Minima

$$R_L = R_{Th}$$





* When load supplies to R_{Th} instead of voltage source, then R_{Th} comes in $-V_o$.

FIRST ORDER CIRCUITS

Electrical energy storage system

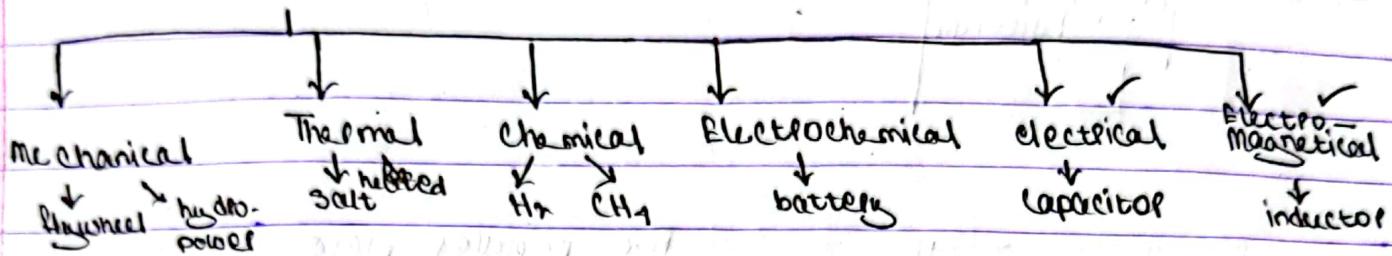


CAPACITORS

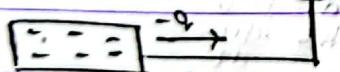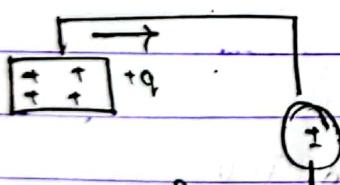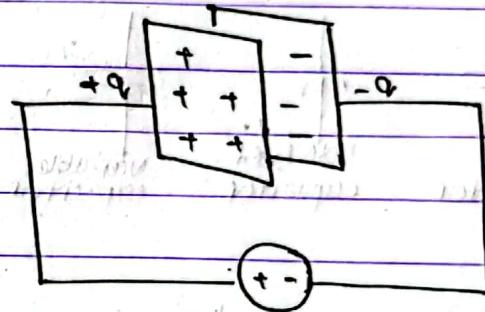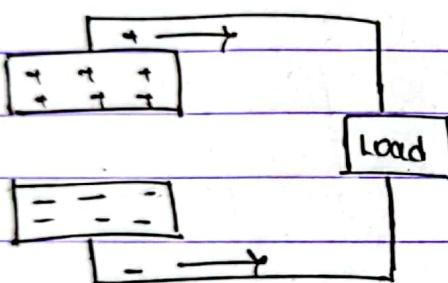

* +ve charge of plate is attracted to negative terminal and the bottom plate is very charged.

* -ve charge of top is attracted to positive terminal, and the top plate is very charged.

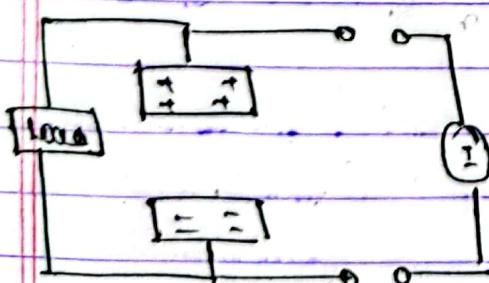* When the plates are fully charged, the voltage source is disconnected.




$$\Theta C = qV \quad q \propto V$$


$$(CV = q)$$

$$\text{Period (T)}$$

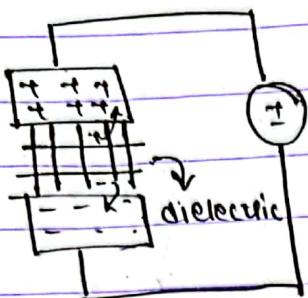
* Capacitance can be increased by increasing surface area of plate. Increasing surface area, increases charge
 ② by using dielectric material.



$$\frac{EdV}{d}$$

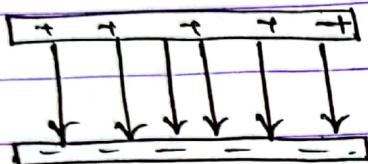

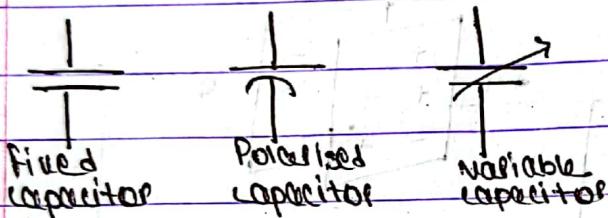For parallel plate capacitor,
 $C = \frac{EA}{d}$ permittivity



$$C = \frac{Q}{V}$$

$$Q = CV$$

$$\frac{dQ}{dt} = C \frac{dV}{dt}$$

$i = C \frac{dV}{dt}$ \rightarrow capacitor does not have fixed $i-v$ characteristics. It depends on the $\frac{dV}{dt}$

$$V(t) = \frac{1}{C} \cdot \int i(t) dt \Rightarrow V(t) = \frac{1}{C} CV^0 - \frac{1}{2} CV_0^2$$


$$\text{power} = P = VI = CV \frac{dV}{dt}$$

$$\text{stored energy, } W(t) = \frac{1}{2} CV^2 - \frac{1}{2} CV_0^2$$

Final \leftarrow Initial voltage
Voltage of capacitor of capacitor

Properties of capacitor

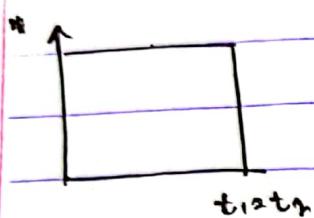
* When a dc voltage capacitor is connected to a dc supply, voltage across capacitor is constant and current is 0. Thus, an open circuit is formed.



$$\Delta t = t_2 - t_1 = 0$$

$$i = C \frac{dV}{dt} = \lim_{\Delta t \rightarrow 0} \frac{\Delta V}{\Delta t} = \frac{\Delta V}{0} \rightarrow \infty$$

SOURCE-FREE RC CIRCUIT

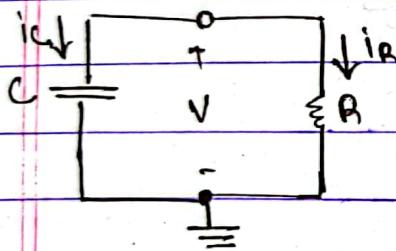

$$V = V_0 e^{-\frac{t}{RC}} \quad \text{At } t=0, V(0) = A = V_0$$

$$V(t) = V_0 e^{-\frac{t}{RC}}$$

$$V(t) = V_0 e^{-\frac{t}{T}}$$


$$\text{At } t = T$$

$$V(t) = V_0 e^{-\frac{T}{2}}$$


$$= V_0 e^1$$

$$= 0.3681 V_0$$


$$= 36.8\% V_0$$

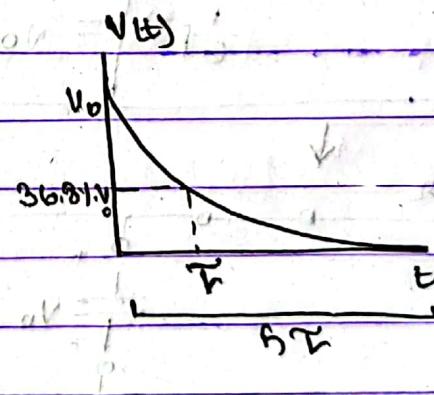

T is the time when the discharging voltage is decreased to 36.81% of its initial voltage.

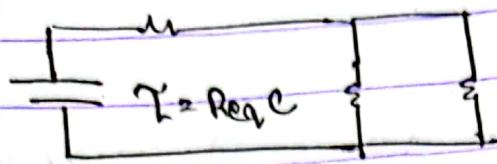

Problem 7

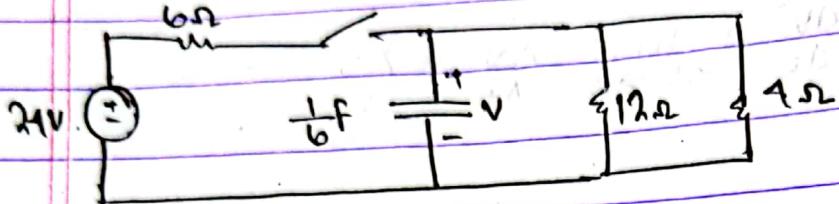



source free

voltage across a capacitor

$$V(t) = V_0 e^{-t/RC}$$

$$Z = R_{\text{eq}} \times C \quad (t \neq 0)$$

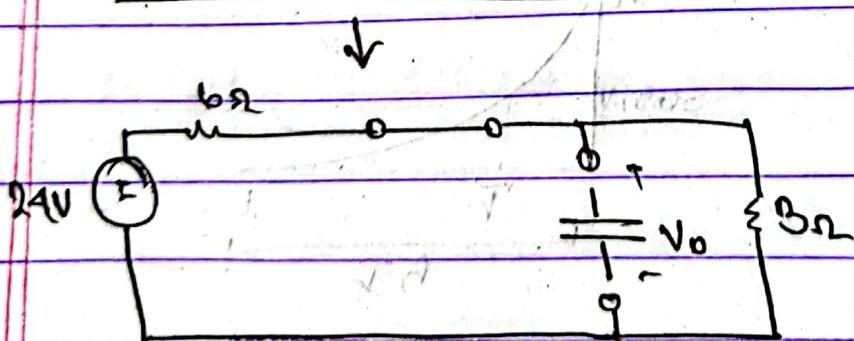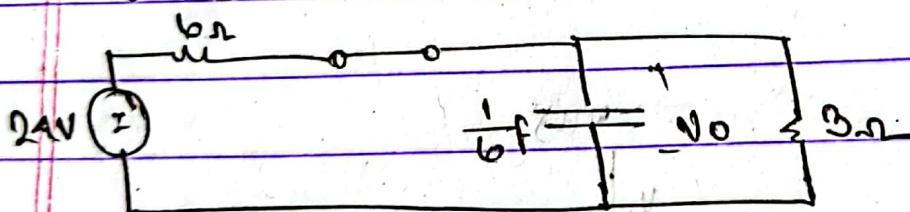
$t > 0 \rightarrow$ time before the switch is opened.



$$i_2 C \frac{dV}{dt} = 0 \quad (\text{open})$$

$$V_0 = \frac{3}{3+6} \times 24 = 8V$$

tr 0

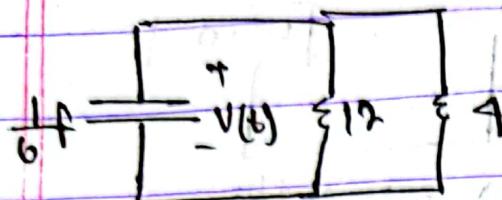



$$T = (Req) \times C = (12 \parallel 1) \times \frac{1}{6} = \frac{1}{2} \text{ s}$$

$$V(t) = 8e^{\frac{1}{2}t} + 8e^{-2t} (V)$$

$$W = \frac{1}{2} CV_0^2 = \frac{1}{2} \left(\frac{1}{6}\right) (0)^2 = 6.333 \text{ J}$$


MONDAY

Problem - 3

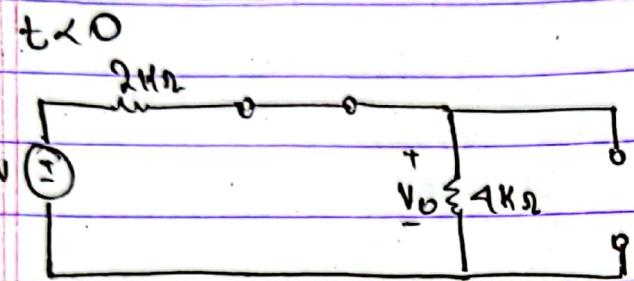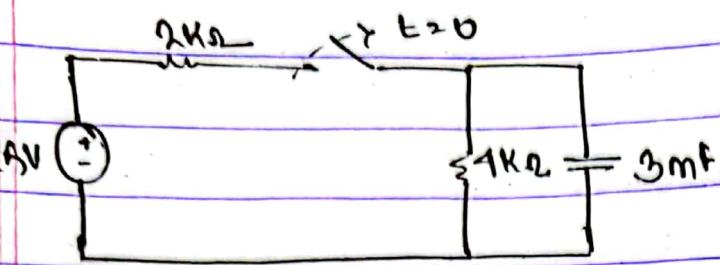

$$V_o = \frac{4k}{2k + 4k} \times 10 = 10V$$


t > 0

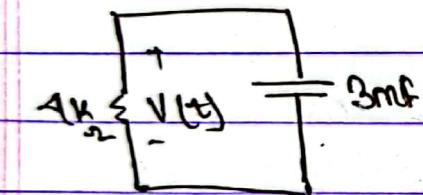

$$T = R_{eq} C \Rightarrow (4 \times 10^3) \times (3 \times 10^{-3}) = 12 \text{ s}$$

$$V(t) = V_o e^{-\frac{t}{T}}$$
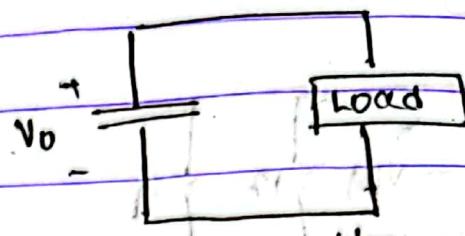
$$V(t) = 10e^{-\frac{t}{12}} \text{ (V)}$$




$$t > 0 \quad \begin{cases} V(t) = V_o e^{-\frac{t}{T}} \\ T = R_{eq} C \end{cases}$$

$$W = \frac{1}{2} C V_o^2 \quad W = \frac{1}{2} C V_o^2 e^{-2t/T}$$

↳ stored E in capacitor at any time t.

$$\begin{aligned} & \text{E transferred to load over time,} \\ & = \frac{1}{2} C V_o^2 - \frac{1}{2} C V_o^2 e^{-2t/T} \\ & = \frac{1}{2} C V_o^2 (1 - e^{-2t/T}) \end{aligned}$$

Problem 3

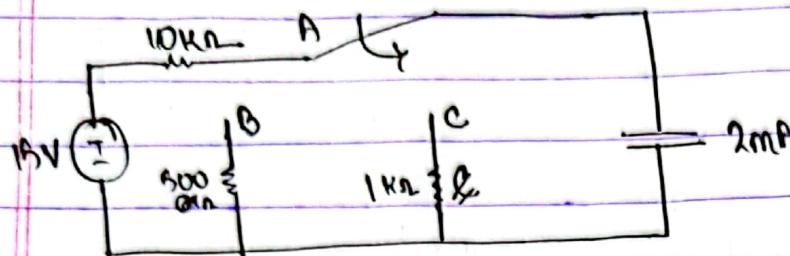


$t > 0$



$$V_o = 15V$$


$t > 0 \quad 1 \neq t > 0$

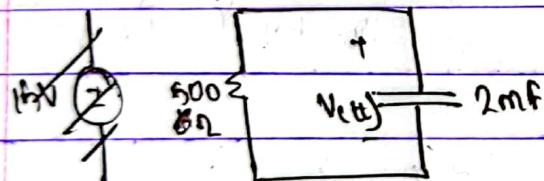

$$15 \times 500 \times 10^{-3} \times 10 \times 10^{-3} = 1000 \times 10^{-3}$$

$$V_o(t) = 15e^{-10t} \quad (V) \quad (for \quad t > 0)$$

$t \leq 1$

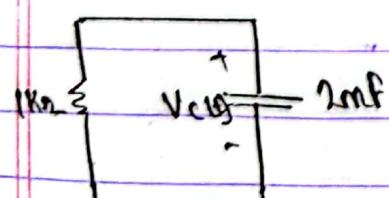

$$V_o(t) = V_0 e^{-t/\tau}$$

From $t > 0$,

$$V_0 = (15e^{-1}) e^{-t/\tau}$$

$$= (15e^{-1}) e^{-t/\tau}$$


$$= 5.52e^{-t/\tau} \quad (t < 1)$$

$$\tau = (1 \times 1000) / (2 \times 10^{-3}) = 200$$

$$= 5.52e^{-t/200} \quad (t < 1)$$

STEP RESPONSE OF A RC CIRCUIT

v_{input}

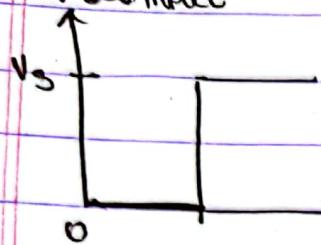

$$V(t) = V_s + (V_0 - V_s) e^{-t/RC}$$

$$V(t) = \begin{cases} V_0 & t < 0 \\ V_s + (V_0 - V_s) e^{-t/RC} & t \geq 0 \end{cases} \Rightarrow V_s$$

$t = 5T$


$$V(t) = 63.7\% (V_s - V_0) + V_0$$

$$V(t) \rightarrow V(\infty) \text{ at } t \rightarrow \infty$$

$$V(t) = V_s + (V_0 - V_s) e^{-t/RC}$$

$\downarrow V(\infty)$ $\downarrow V(0)$
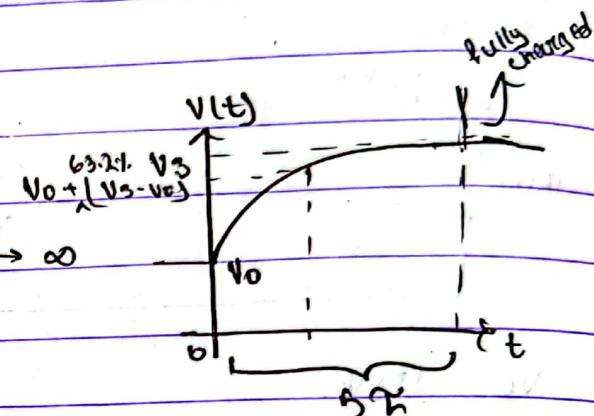
$$V(t) = V(\infty) + (V(0) - V(\infty)) e^{-t/RC}$$




$$V(t) = V_s$$

$0-5V$ } same time
 $5-5V$ } $(5T)$

$T = 5T$


PROBLEM 11

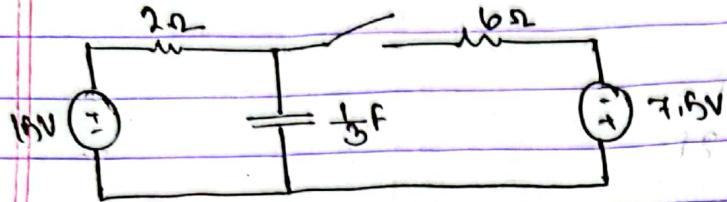

$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/2}$$


$$\text{if } V(\infty) = 0, \text{ source free} \rightarrow V(t) = V(0) e^{-t/2}$$

$t < 0$

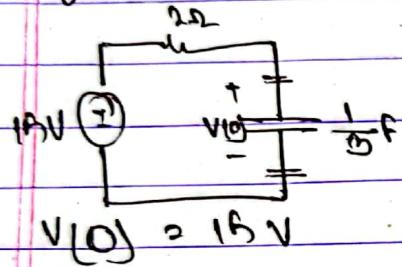

$$V(0) = 15V$$

$t > 0$

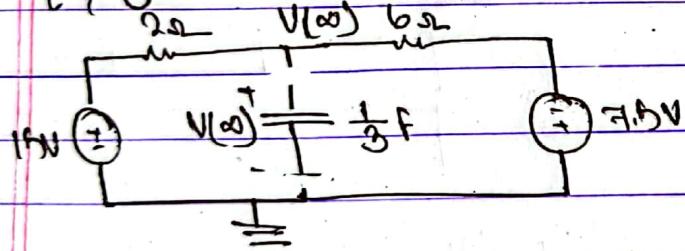

* If there is any independent DC source, then the capacitor will be open.

$$\frac{V(\infty) - 15}{2} + V(0) + \frac{7.5}{6} = 0$$

$$\frac{2}{3}V(\infty) + \frac{25}{12} \Rightarrow V(0) = 9.375V \approx 9.375V$$


$$T = (2 \times 6) \times \frac{1}{3} = (1.5) \left(\frac{1}{3}\right) = \frac{1}{2} \approx 0.5s$$

$$V(t) = 9.375 + (15 - 9.375)e^{-t/0.5}$$


$$V(t) = 9.375 + 5.625e^{-t/0.5}$$

$$V(0.5) = 9.375 + 5.625e^{-0.5/0.5} = 11.49V$$

Problem 13

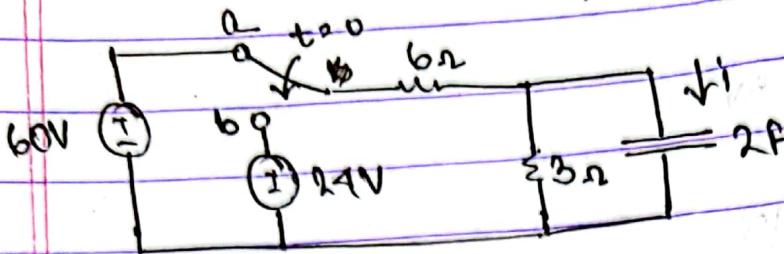


$t < 0$

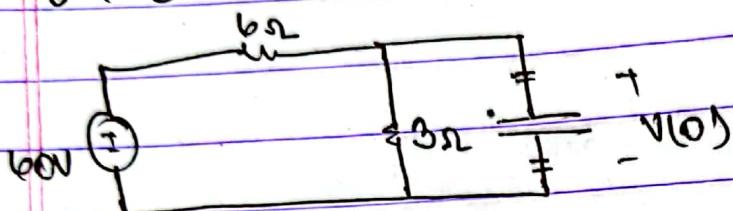

$$V(0) = \frac{3}{3+6} \times 60 = 20 \text{ V}$$

$t > 0$

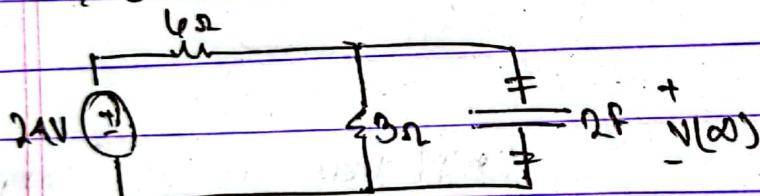

$$V(\infty) = \frac{3}{6+3} \times 24 = 8 \text{ V}$$

$$T = (b \parallel 3) \times C = 1.3$$

$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-\frac{t}{T}}$$

$$= 8 + [20 - 8] e^{-\frac{t}{1.3}}$$

$$V(t) = 8 + 12 e^{-0.769t}$$



$$i(t) = C \frac{dV}{dt}$$

$$= C \frac{d}{dt} (8 + 12 e^{-0.769t})$$

$$= 2 \left[12 (-0.769) e^{-0.769t} \right]$$

$$i(t) = 6 e^{-0.769t} \text{ (A)}$$


Problem 14

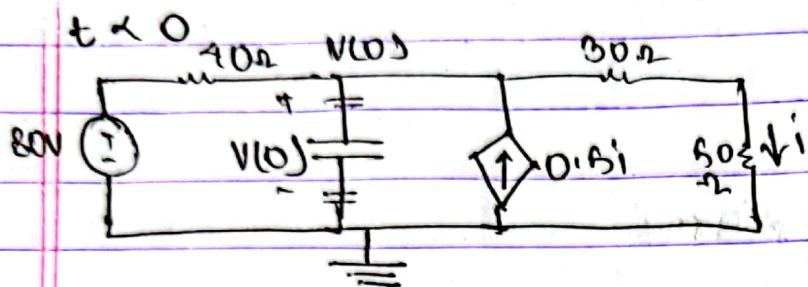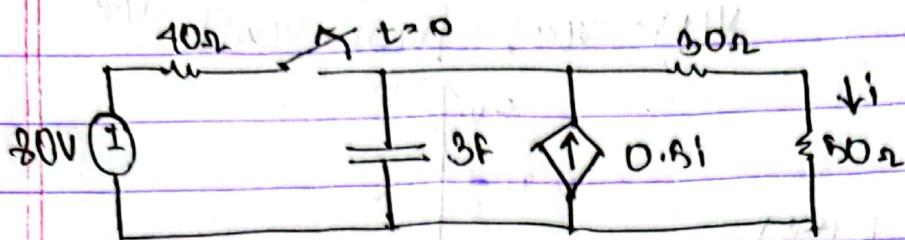

$$\frac{V(0) - 80}{40} + \frac{V(0)}{80} = 0.5i \quad i = \frac{V(0) - 80}{80}$$


$$\frac{V(0) - 80}{40} + \frac{V(0)}{80} = 0.5 \frac{V(0)}{80}$$
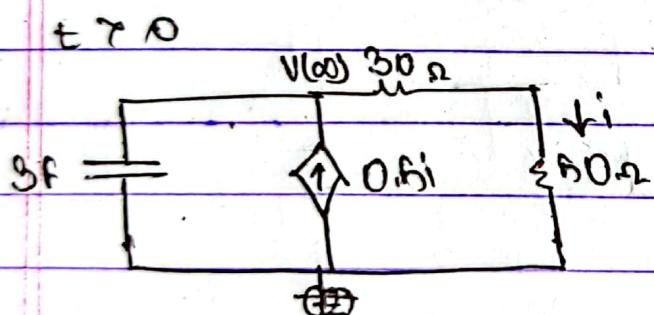
$$V(0) = 106.67 \text{ V} \quad (t < 0)$$



$$V(0+) = 0 \text{ V}$$

$$i(\infty) = 0 \text{ A}$$

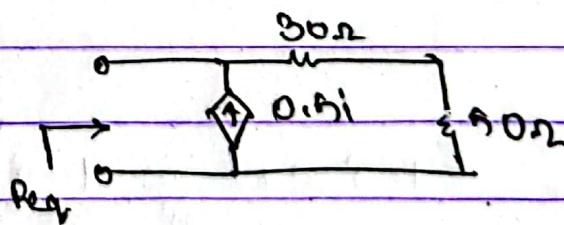


CTURA

DATE: 07/12/20

WEDNESDAY


Problem 1b

(i)

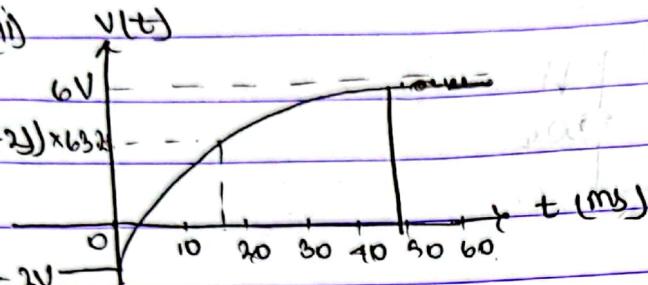

$$6T = 4b \Rightarrow T = 9 \text{ ms}$$
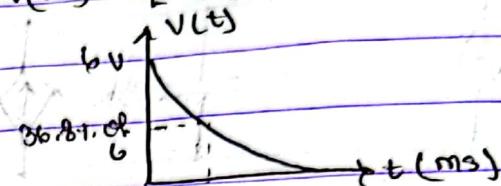
$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/T}$$



(ii) $V(\infty) = 6V, V(0) = -2V, T = 9 \text{ ms}$

$$V(t) = 6 + [-2 - 6] e^{-t/9}$$

$$= 6 - 8 e^{-t/9}$$

(iii) $U_1 = \frac{1}{2} C U_0^2$

$$U_0^2 = \frac{1}{2} (2.25)(-2)^2$$


$$= 4.5 \text{ J} \approx 2 \text{ J}$$

$$2 \text{ J} = 2 \times 9 \times C$$


$$9 = 2 \times 2.25 \times C$$

$$C = 2.25 \text{ } \mu\text{F}$$


(iv)

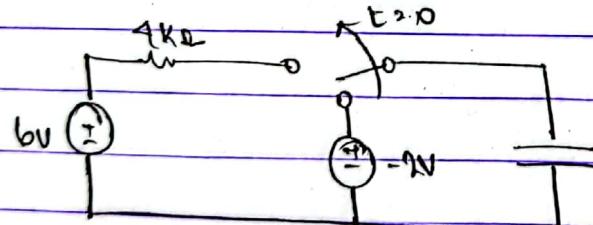

Problem 16

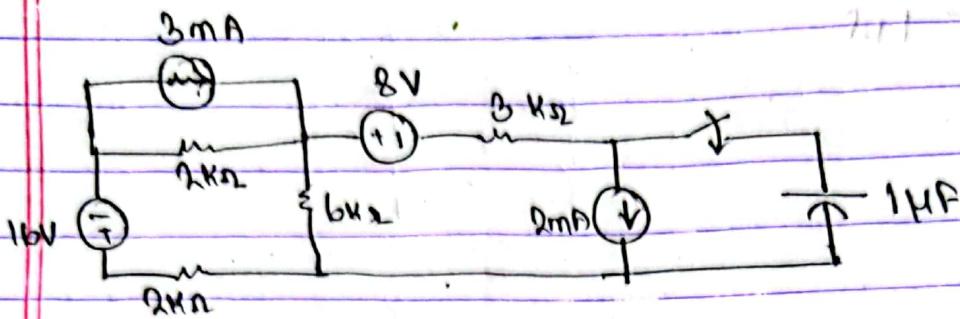


$R_{TH} \rightarrow$

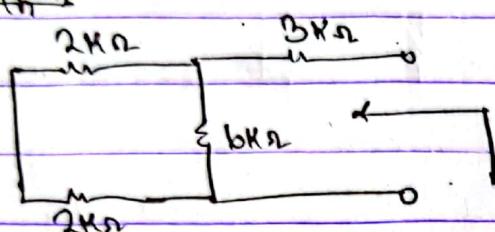

$$R_{TH} = (2 + 2) \parallel 6 + 3 = 5 \cdot 4 \text{ k}\Omega$$

V_{TH}

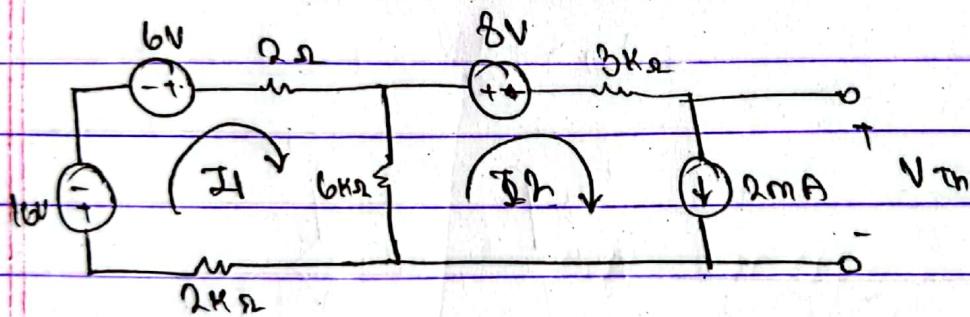

$$I_2 = 2 \text{ A}$$

$$16 - 6 + 2I_1 + 6(I_1 - I_2) + 2I_1 = 0$$

$$10I_1 - 6I_2 = 10$$


$$16 - 6 + 10I_1 - I_2 = 0 \quad \text{--- (1)}$$

$$10I_1 - 6I_2 = 10 \quad I_2 = 2$$

$$I_1 = 0.2 \text{ mA}$$

$$-V_{TH} - 3I_2 - 8 + 6(I_1 - I_2) = 0$$

$$V_{TH} = -24.8 \text{ V}$$

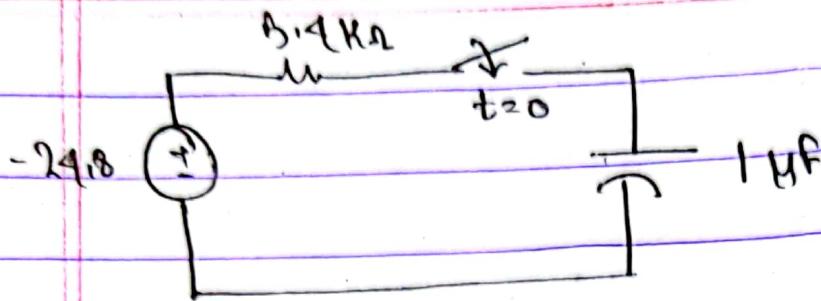

$$t < 0, V(0) = 0 \text{ V}$$

$$t > 0, V(\infty) = -24.8$$

$$Z = R_{eq} \times C \approx 5.4 \text{ m}\Omega$$

$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/5.4}$$

$$= -24.8 [1 - e^{-t/5.4}]$$

$$V(t) = -24.8 + 24.8 e^{-t/5.4}$$

$$i(t) = C \frac{dV}{dt} = 10 \times \frac{-24.8 e^{-t/5.4}}{5.4}$$

$$i(t) = 10 \times \frac{-24.8}{5.4} e^{-t/5.4}$$

INDUCTORS

$$F = \frac{1}{4\pi\epsilon} \frac{Qq}{r^2}$$

$$F = -qE$$

$$E = \frac{1}{4\pi\epsilon} \frac{Q}{r^2}$$

\vec{E} & \vec{H} are same \vec{D} and \vec{B} are same

\vec{E} \vec{H}

$$D = \epsilon E$$

Electric field density



\vec{B} \vec{H}

$$B = \mu H$$

magnetic field density

$$B = \frac{\Phi}{A} \quad (Wb/m^2 = T = 10^4 \text{ Gauss})$$

Faraday's law.

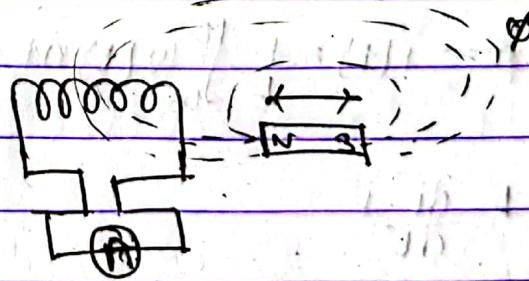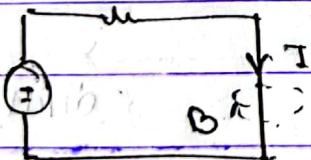

* An electric field can produce a magnetic field. But, a magnetic field can produce an electric field with a moving or changing magnetic field.

* To create changing magnetic field, we have to move either the magnet / coil or perpendicularly.

Inductance

$$\Phi \propto I$$

$$\Phi = L I$$

↓
inductance

$$N\Phi = L I$$

- * L does not depend on Φ and I as increasing I , increases Φ
- * L depends on length, surface area, material

Lenz's law


$$\frac{d\Phi}{dt} = -\frac{L}{N} \frac{dI}{dt}$$

$$C_2: L \frac{dI}{dt}$$

— x — x —

$$N = L \frac{di}{dt}$$
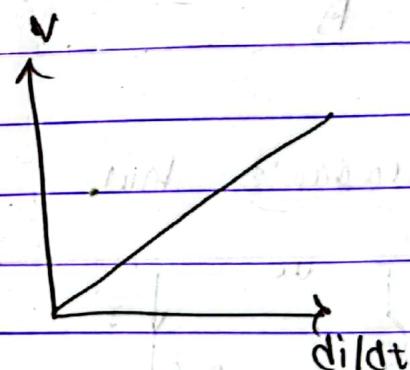
$$H(t) \rightarrow \frac{1}{L} \int_{t_0}^t i(t) dt = \frac{1}{L} \int_{t_0}^t v(t) dt + v(t_0)$$



$$P = V_{\text{loss}} = L \frac{di}{dt} i$$

$$W(t) = \frac{1}{2} L i^2$$

current
cannot be
found out
directly

$$I_C = N \frac{dV}{dt}$$

voltage
cannot
be found directly

$$I_{\text{ext}} = V_L = L \frac{di}{dt}$$

$$W = \frac{1}{2} C V^2$$

$$V(t) = V(0) + [V(0) - V(0)] e^{-\frac{t}{RC}}$$

$$I(t) = I(0) + [I(0) - I(0)] e^{-\frac{t}{RC}}$$


C open at DC

$$W = \frac{1}{2} L I^2$$


$$T = \frac{L}{R_{\text{ext}}}$$

L short at DC

Problem 6

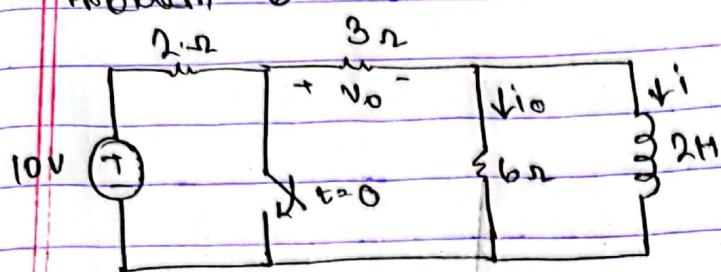


$t < 0$

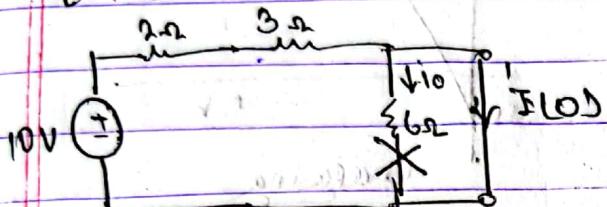

$$I(0) = \frac{10}{2+3} = 2 \text{ A}$$

$t > 0$

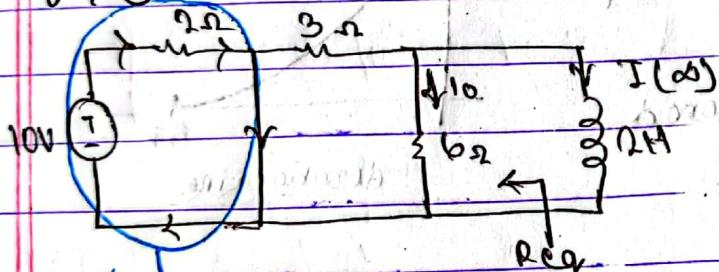


is shorted
so no contribution
in the circuit anymore
to find $I(\infty)$

$$R_{\text{eq}} = 6/13 = 0.46 \text{ Ω}$$

$$T = \frac{L}{R_{\text{eq}}} = \frac{2}{0.46} = 4.35 \text{ ms}$$

$$I_t = I_0 e^{-\frac{t}{T}}$$

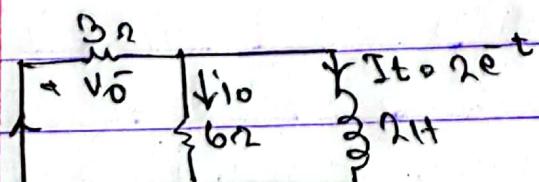

$$I_0 = \frac{3/16}{0.46} \times 10 e^{-\frac{t}{T}} = \frac{2}{0.46} (2 e^{-\frac{t}{T}}) = \frac{2}{0.46} \frac{1}{3} e^{-\frac{t}{T}}$$



$$V_o = \frac{1}{2} (I_t - I_0) \times R_3 = \frac{1}{2} (2 e^{-\frac{t}{T}} - \frac{2}{0.46} \frac{1}{3} e^{-\frac{t}{T}}) \times 3$$

MONDAY


RL CIRCUITS

$$I(t) = I(0) + [I(0) - I(\infty)] e^{-\frac{t}{T}}$$

$$T = \frac{L}{R_{\text{eq}}}$$

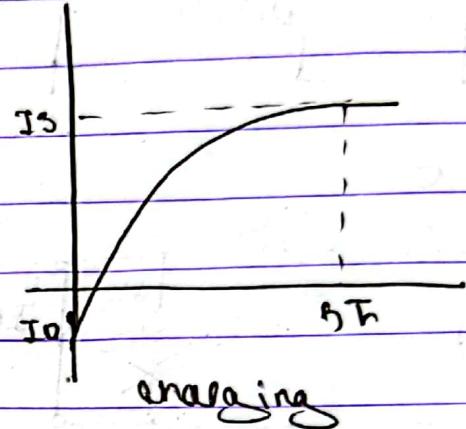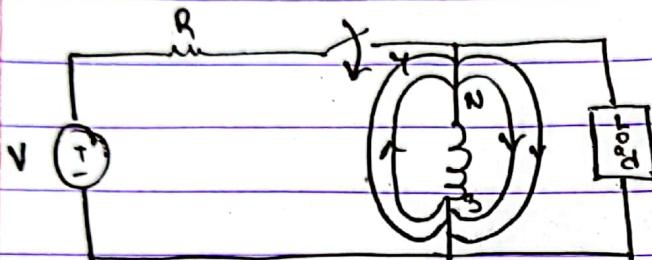


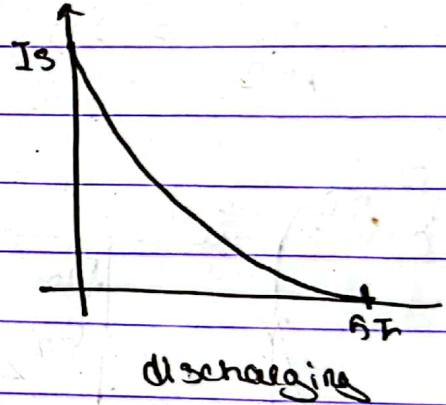
- * Inductor current can't be turned off abruptly.
- * Current in inductor needs a closed loop.
- * When an inductor is open circuit, a spark is created at the opened switch to make the current 0.



$$U_C = \frac{1}{C} \int I(t) dt \left[e^{-\frac{t}{RC}} \right] \rightarrow \text{capacitor}$$

$$U_L = \frac{1}{L} \int I(t) dt \left[e^{-\frac{t}{RC}} \right] \rightarrow \text{inductor}$$


Problem 7

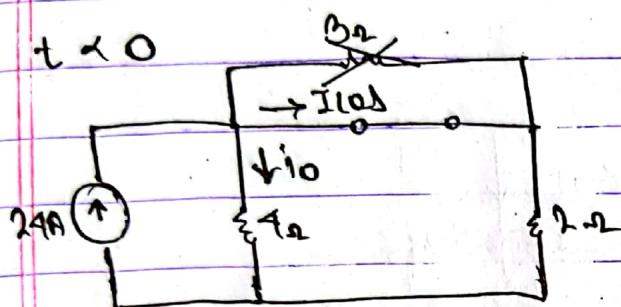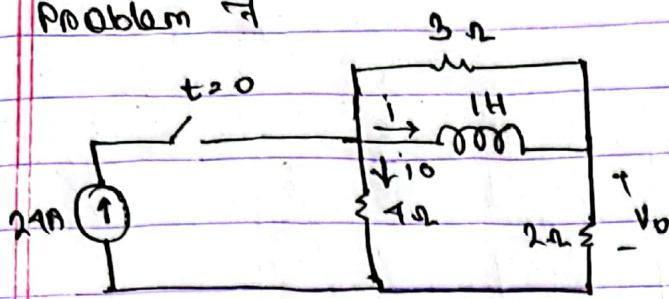

$$i(0) = \frac{24}{3} = 8A$$

$$V_0 = 24 - 8 \cdot 2 = 8V$$

$$i_0 = 24 - 16 = 8A$$

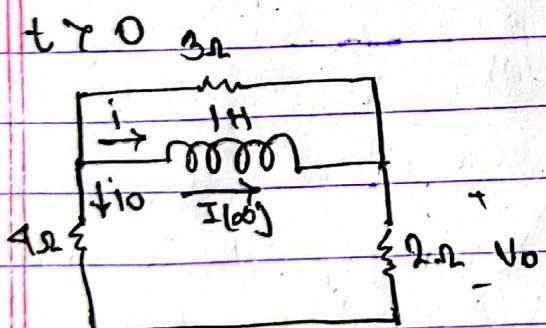

$$i(\infty) = 0A$$


$$T = \frac{1}{R_{eq}} = \frac{1}{(4+2)\parallel 3} = 0.3333s$$

$$i(t) = 16e^{-2t}$$


$$i_0 = \frac{316}{6} \times 16e^{-2t} = -\frac{16}{3}e^{-2t} \text{ (A)}$$

$$V_0 = -i_0 \times 2 = \frac{16}{3}e^{-2t} \times 2 = \frac{32}{3}e^{-2t} \text{ (V)}$$

Problem 19

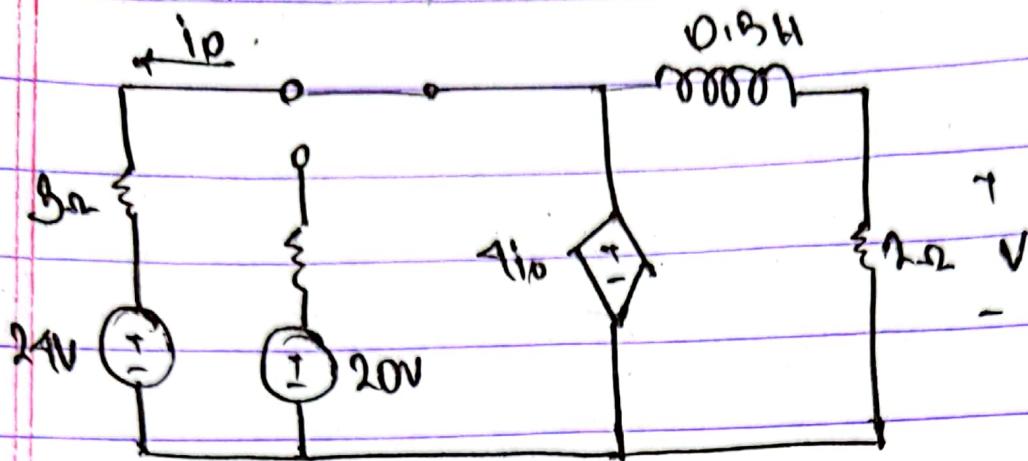

$t < 0$

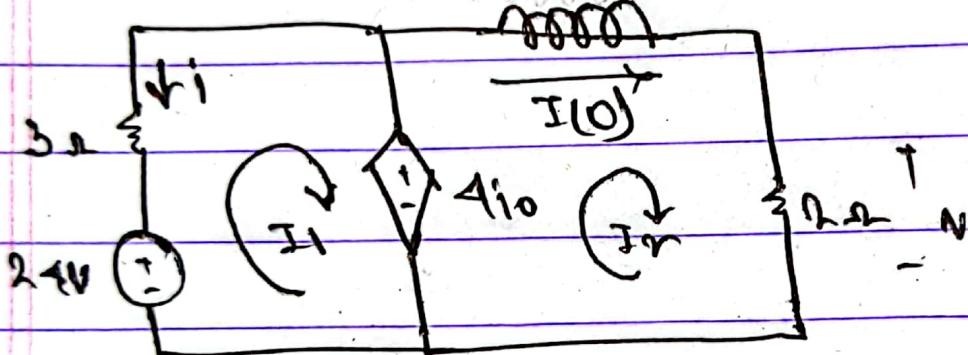

$$-24 + 3I_1 + 4i_{10} = 0 \quad i_{10} = I_1$$

$$-24 + 3I_1 - 4I_1 = 0$$

$$I_1 = -24A \quad i_{10} = 24A$$

$$-4i_{10} + \overline{I(0)} + 2I_2 = 0$$


$$-4I_1 + 2I_2 = 0$$

$$I_2 = 48A$$

$$I(0) = I_2 = 48A$$

$$V_0 = 2 \times I(0) = 2 \times 48 = 96V$$


$t = 0$

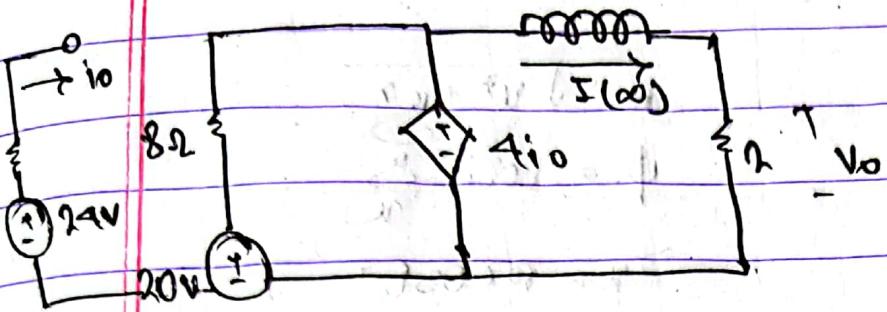

$i_0 = 0$

$i_{0,0} = 0$ (Dependent source is shorted out)

$$I(0) = 0A$$

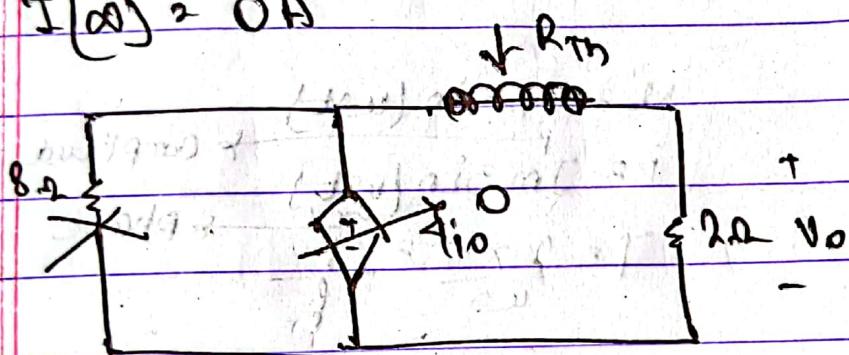

$$R_m = 2\Omega$$

$$T = \frac{L}{R_m} = \frac{0.8}{2} = 0.4$$

$$I(t) = 48e^{-\frac{t}{0.4}} = 48e^{-2.5t}$$

$$V_o = 2(48e^{-2.5t}) = 96e^{-2.5t} \text{ (V)}$$

AC FUNDAMENTALS AND AC CIRCUITS

Complex Numbers

$z = x + iy$ → Rectangular form

$z = r \angle \theta$ → Polar form

$z = r e^{j\theta}$ → Exponential form

$$r = \sqrt{V^2 + U^2}$$


$$\theta = \tan^{-1} \frac{U}{V}$$

$$V = r \cos \theta$$

$$U = r \sin \theta$$

$$V + jU = r (\cos \theta + j \sin \theta)$$

Arg

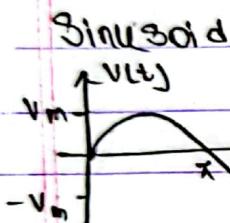

$$V = V_m \sin(\omega t)$$

→ amplitude

$$i = I_m \sin(\omega t)$$

→ phase



$$T = \frac{2\pi}{\omega} = \frac{1}{f}$$

* A circular motion provides sinusoidal voltage.


$$* 50 \text{ Hz} = 50 \text{ cycles/sec}$$

Leading & Lagging Sinusoid


$$V(t) = V_m \sin(\omega t + \phi)$$

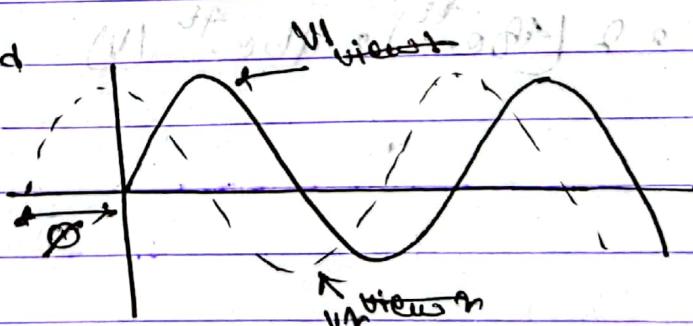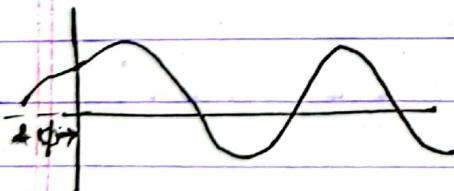

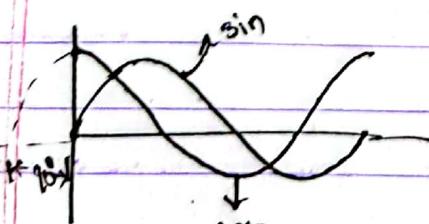- * V₂ leads V₁ by ϕ
- * V₂ lags V₁ by $(360^\circ - \phi)$
- * V₂ leads V₁ by $360^\circ - \phi$



+ coswt

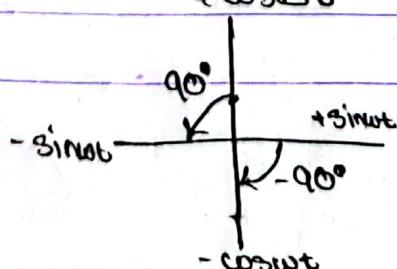

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

18(iii) Problem 3

$$I_m \cos(\omega t + \phi)$$

$$(iii) I_3 = -20 \cos(314t - 30^\circ)$$

$$\text{amp} = 20 \text{ (A)}$$

$$\omega = 314 \text{ rad/s}$$

$$\omega = 2\pi f$$

$$f = \frac{314}{2\pi}$$

$$T = \frac{1}{f} = \frac{1}{\frac{314}{2\pi}} = \frac{2\pi}{314}$$


$$20 \cos(314t - 30^\circ + 180^\circ)$$

$$= 20 \cos(314t + 180^\circ)$$

$$\downarrow \phi$$

LECTURE

Problem 1

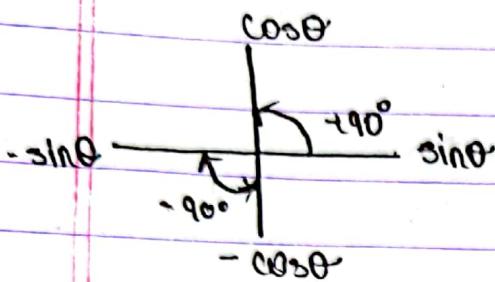


$$(i) v(t) = 10 \cos(4t - 60^\circ)$$

$$= 10 \sin(4t - 60^\circ + 90^\circ)$$

$$= 10 \sin(4t + 30^\circ)$$

$$i(t) = 4 \sin(4t + 60^\circ)$$

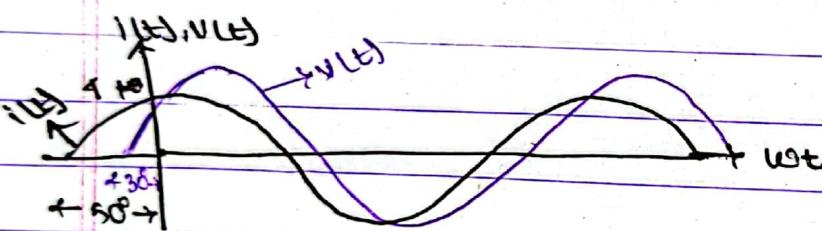* from cos to sin, we are going 90° backward.
To compensate for the backward 90° , we add 90°
[$\cos \sin \theta + 90^\circ = \cos \theta$]



i leads v by 20°

OR

$$i(t) = 4 \sin(4t + 60^\circ)$$

$$= 4 \cos(4t + 60^\circ - 90^\circ)$$

$$= 4 \cos(4t - 30^\circ)$$

$$[\sin(\cos \theta - 90^\circ + \sin \theta)]$$

$$(iv) i_1(t) = -4\sin(377t + 90^\circ) \quad i_1(t) = 4\cos(377t - 60^\circ)$$

$$= 4\cos(377t + 90^\circ + 90^\circ)$$

PHASOR

$$Z = R + jL = 1 + j2 = \sqrt{5} \angle 63.4^\circ$$

$$(\cos\theta + j\sin\theta)$$

$$V(t) = V_m \cos(\omega t + \phi)$$

$$= \text{Re} \{ V_m e^{j(\omega t + \phi)} \}$$

$$= \text{Re} \{ V_m \{ \cos(\omega t + \phi) + j\sin(\omega t + \phi) \} \}$$

$$= \text{Re} \{ V_m e^{j\omega t} e^{j\phi} \}$$

$$= \text{Re} \{ V_m e^{j\phi} e^{j\omega t} \}$$

$$= \text{Re} \{ V e^{j\omega t} \}$$

$$V_m \cos(\omega t + \phi)$$

$$\text{phasor, } V = V_m e^{j\phi} = V_m \angle \phi$$

$$I = V / Z = V_m \angle \phi / (R + jL)$$

$$= V_m \angle \phi$$

Complex mode

MODE 2

1 2 3 ENG =

OPTN 1 2 3 4 =

AC ANS =

Problem 5

$$(1) -14 \sin(\beta t - 220^\circ)$$

$$= -14 \sin(\beta t - 220^\circ + 180^\circ)$$

$$= 14 \sin(\beta t + 160^\circ) = 14 \angle 160^\circ$$

$$(2) -20 \cos(314t - 30^\circ)$$

$$= 20 \cos(314t - 30^\circ + 180^\circ)$$

$$= 20 \cos(314t + 150^\circ) = 20 \angle 150^\circ$$

PHASOR RELATIONSHIPS FOR CIRCUIT ELEMENTS (P)

Resistor,

$$i(t) = I_m \cos(\omega t + \phi)$$

$$v(t) = R I_m \sin(\omega t + \phi) = \frac{1}{2} I_m \cos(\omega t + \phi)$$

$$v = R I_m \angle \phi \quad \begin{matrix} \uparrow \\ \text{no } \phi \end{matrix} \quad v = R I \quad \begin{matrix} \uparrow \\ \text{phasor} \end{matrix}$$

Inductor

$$i(t) = I_m \cos(\omega t + \phi)$$

$$v(t) = \omega L \frac{di}{dt} = -L I_m \sin(\omega t + \phi) \quad \begin{matrix} \uparrow \\ \sin \rightarrow -\cos \end{matrix}$$

$$= -\omega I_m \cos(\omega t + \phi - 90^\circ)$$

$$= \omega I_m \cos(\omega t + \phi - 90^\circ + 180^\circ) \quad \begin{matrix} \uparrow \\ -\cos \rightarrow \cos \end{matrix}$$

$$= \omega I_m \cos(\omega t + \phi + 90^\circ)$$

Phase form, $V = \omega L I_m \angle \phi + 90^\circ$

$$V = \omega L I_m \angle \phi e^{j90^\circ}$$

$$V = j\omega L I_m \angle \phi \quad V = j\omega L I$$

R

$$V = RI$$

complex number

h

$$V = j\omega h I$$

resistance

$$DC, W = 0$$

$$L, R = 0 \quad C, R = \infty$$

$$V = V_m \angle \theta$$

$$I = I_m \angle \theta$$

Impedance

$$\frac{V}{I} = R$$


$$\frac{V}{I} = j\omega h$$

$$\frac{V}{I} = \frac{1}{j\omega C}$$


* Impedance depends on frequency of

Impedance

$$Z_L = j\omega h \quad | Z_C = \frac{1}{j\omega C}$$

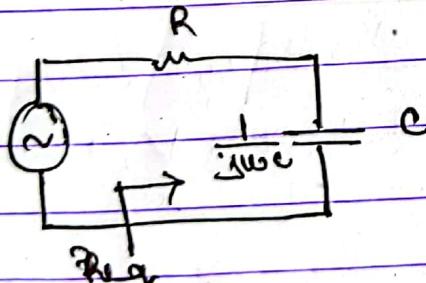

$$Z_{eq} = R + \frac{1}{j\omega C}$$

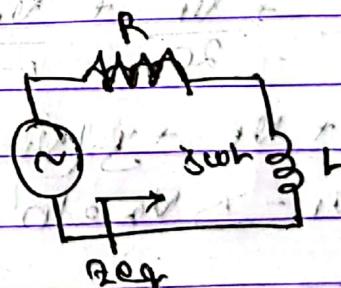


$$Z_{eq} = R + j\omega h$$

No AC circuit can have only DC + AC

④ General response of + AC (AC + DC)

Problem 7

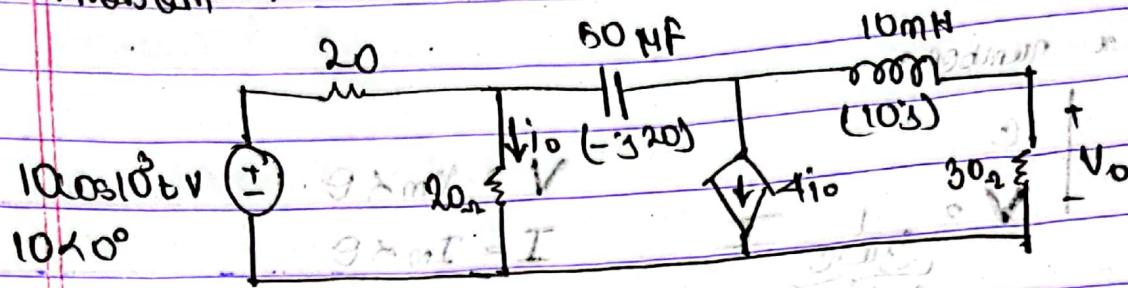

Impedance of $60\mu F$ capacitor

$$V = 8.96 \text{ mV} \text{ (wt)}$$

$$Z_C = \frac{1}{j\omega C}$$

$$= \frac{1}{j \times 1000 \times 60 \times 10^{-6}} = -20j$$

$$Z_C = j\omega C$$

$$= j \times 1000 \times 10 \times 10^{-3} = 10j$$

KCL at node 1,

$$\frac{V_1 - 10 \angle 10^\circ}{20} + \frac{V_1 - V_r}{20} + \frac{V_1 - V_r}{(-20j)} = 0$$

$$\Rightarrow V_1 - 10 + V_1 + j(V_1 - V_r) = 0$$

$$\Rightarrow (1 + j) V_1 - j V_r = 10 \quad \text{--- (1)}$$

KCL at node 2,

$$A_{10} + \frac{V_r - V_1}{-j20} + \frac{V_r - 0}{30 + j10} = 0$$

$$4 \times \frac{V_1}{20} + \frac{V_2 - V_1}{-j20} + \frac{V_r}{30 + j10} = 0$$

$$\Rightarrow 0.2 V_1 + \frac{0.05(V_r - V_1) + (0.03 - j0.01) V_r}{30 + j10} = 0$$

$$(0.2 - j0.05) V_1 + (0.03 + j0.08) V_r = 0 \quad \text{--- (11)}$$

Cramer's Rule

$$\Delta = \begin{bmatrix} 2+j & -j \\ j & 0.03+j0.01 \end{bmatrix} \Rightarrow \Delta = 0.07+j0.01$$

$$\Delta_{12} = \begin{bmatrix} 10 & -j-j \\ 0 & 0.03+j0.01 \end{bmatrix} \Rightarrow \Delta_1 = 0.3+j0.4$$

$$\Delta_{22} = \begin{bmatrix} 2+j & 10 \\ 0.2-j0.08 & 0 \end{bmatrix} \Rightarrow \Delta_2 = -2+j0.6$$

$$V_1 = \frac{\Delta_{12}}{\Delta} =$$

$$V_2 = \frac{\Delta_{22}}{\Delta} =$$

Problem 11

KCL at nodes 1 & 2,

$$\frac{V_1}{R} + \frac{V_1 - V_3}{4\pi\text{rad}} + \frac{V_0}{1} + \frac{V_2 - V_3}{1} = 0$$

At node 3,

$$\frac{V_3}{1} + \frac{V_3 - V_1}{4\pi\text{rad}} + \frac{V_3 - V_2}{1} = 0 \quad (1)$$

KCL at node 3,

$$0.2V_0 + \frac{V_3 - V_1}{4} + \frac{V_3 - V_2}{1} = 0 \quad (2)$$

$$0.2V_0 = \frac{V_3 - V_1}{4} + \frac{V_3 - V_2}{1} \quad [V_0 = V_1] \quad (3)$$

$$V_1 - V_2 = 12 \angle 0^\circ \quad (4)$$

$$\Delta = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

$$A_1 = \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix}, A_2 = \begin{bmatrix} 0 \\ 1 \\ 0 \end{bmatrix}, A_3 = \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix}$$

$$V_1 = \frac{\Delta A_1}{A_1 \Delta} =$$

$$V_2 = \frac{\Delta A_2}{A_2 \Delta}$$

$$V_0 = \frac{\Delta}{A_3 \Delta}$$

$V_0 =$


$$100 = 7.687 \angle 50.19^\circ$$

$$= 7.687 \cos(\omega t + 50.19^\circ)$$


MONDAY

DATE:

Problem 19

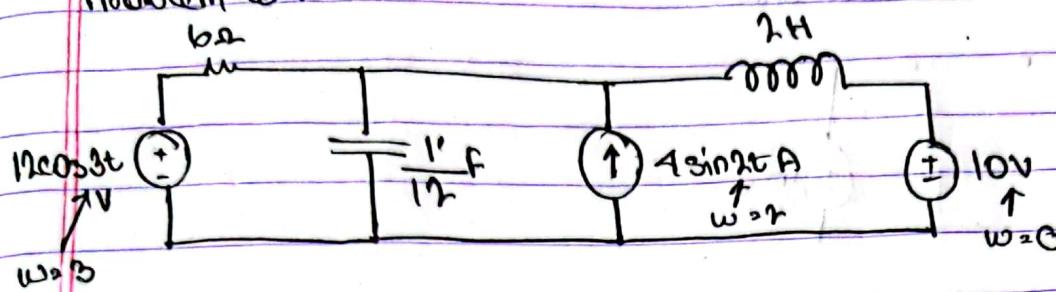

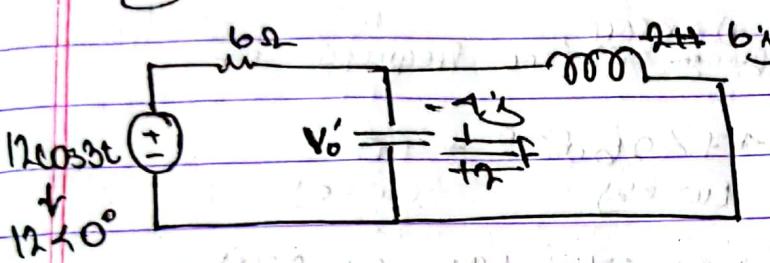Only the $12\cos 3t$ (V) source is active.



$$\frac{1}{12} F = \frac{1}{j \times 3 \times \frac{1}{12}} = 2 - j4$$


$$2H = j \times 3 \times 2 = j6$$

$$V'_0 = \frac{(-j4 \parallel j6)}{(-j4 \parallel j6) + 6} \times 12 \angle 0^\circ$$

$$V'_0 = \left(\frac{1}{5} - \frac{3}{5}j \right) \times 12 \angle 0^\circ$$

$$= 10.43 \angle -26.57^\circ$$

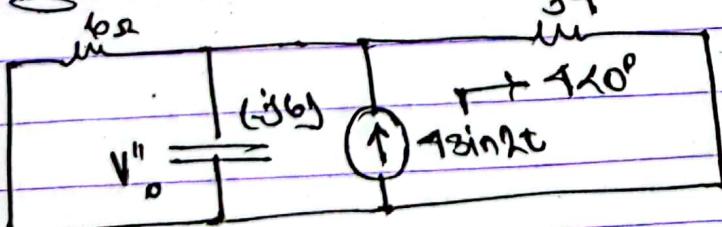
Only the $4\sin 2t$ (A) source is active.



$$\omega = 2 \text{ rad/s}$$

$$\frac{1}{12} F = \frac{1}{j \times 2 \times \frac{1}{12}} = 2 - j6$$


$$2H = j \times 2 \times 2 = j4$$

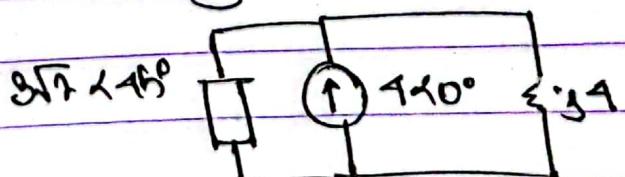

$$V''_0 = \frac{3\sqrt{2} \angle 45^\circ}{2} \times \frac{(3\sqrt{2} \angle 45^\circ \parallel j3)}{3\sqrt{2} \angle 45^\circ} \times 4 \angle 90^\circ$$

$$V''_0 = 21.47 \angle 26.57^\circ \text{ current}$$

Only 10V source is active.

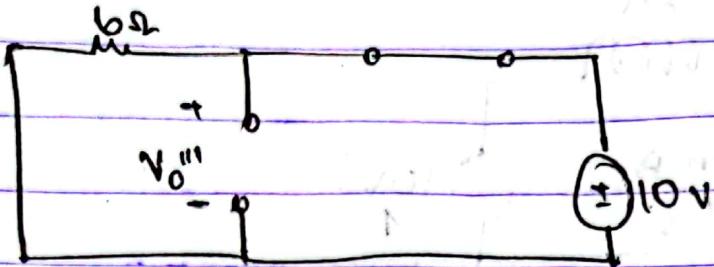

$$V_o''' = 10 \text{ V}$$

According to superposition theorem,
 $V_o = V_o' + V_o'' + V_o'''$ * Frequencies different

$$= 10.73 \angle -26.57^\circ + 21.47 \angle 26.57^\circ + 10$$

($\omega = 3$) ($\omega = 2$) ($\omega = 0$)

$$V_o = 10.73 \cos(8t - 26.57^\circ) + 21.47 \sin(9t + 26.57^\circ) + 10$$

*

INSTANTANEOUS POWER

$$P = VI$$

$$P(t) = V(t)I(t)$$

$$= V_m I_m \cos(\omega t)$$

$$P(t) = \underbrace{\frac{1}{2} V_m I_m \cos(\theta_V - \theta_I)}_{\text{Time independent}} + \underbrace{\frac{1}{2} V_m I_m \cos(2\omega t + \theta_V + \theta_I)}_{\text{Time dependent and periodic}}$$

Time independent

Time dependent and periodic

$$\frac{\sum P(t)}{\text{time}} = \frac{\int_0^T P(t) dt}{T} \rightarrow \frac{(VI)}{(S)} = \frac{W}{(J)} = \text{Power}$$

$$P = \frac{1}{2} V_m I_m (\theta_V - \theta_I) \rightarrow \text{(average power)}$$

$$Z = \frac{V}{I} \quad \text{(phasor)}$$



$$Z = R + jX$$

$\theta_V > \theta_I \rightarrow$ Inductive load $\theta_V - \theta_I = 90^\circ$


$\theta_V < \theta_I \rightarrow$ Capacitive load $\theta_I - \theta_V = 90^\circ$

$\theta_V = \theta_I \rightarrow$ Resistive load


* when load has only capacitance, it is a pure capacitor. \rightarrow \square , $\theta_I - \theta_V = 90^\circ$, $Z = j\boxed{C}$, Power = 0

* when load has only inductor, it is a pure inductor. \rightarrow \square , $\theta_I - \theta_V = 90^\circ$, Power = 0

Problem 22

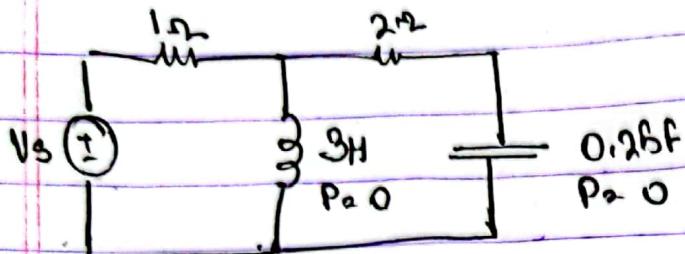

$$V_3 = 8 \cos(2t - 40^\circ)$$

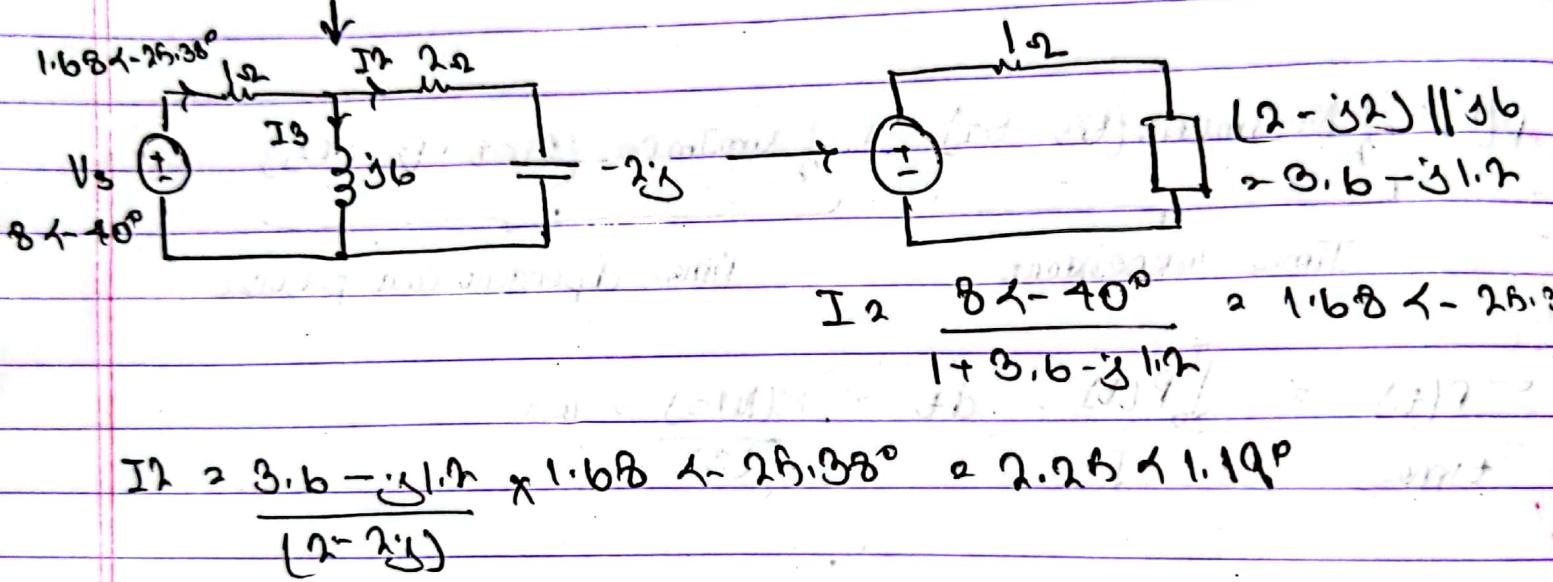


$$I_3 = \frac{3.16 - j1.7 \times 1.68 \angle -26.38^\circ}{3\Omega} = 1.06 \angle -133.66^\circ$$

OR
EFFECTIVE, RMS VALUE

$$P = \frac{1}{T} \int_0^T i^2 R dt = R \frac{1}{T} \int_0^T i^2 dt$$

$$P = I_{\text{eff}}^2 R$$
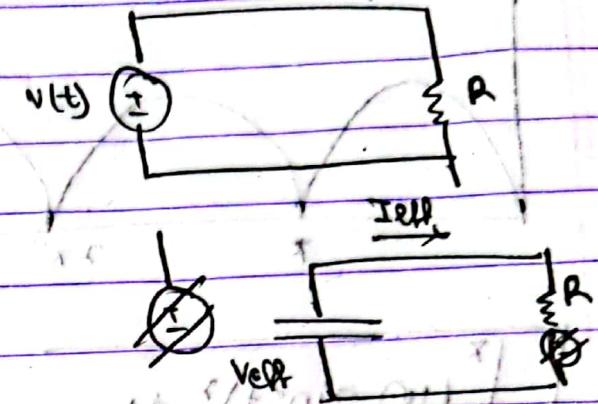
$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$



RMS of value of SINUSOIDS

$$P = I_{\text{rms}}^2 R$$

$$v(t) = V_m \cos(\omega t + \phi)$$

∴


$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$\Rightarrow \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i)$$


$$P = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$$

Problem 2.3

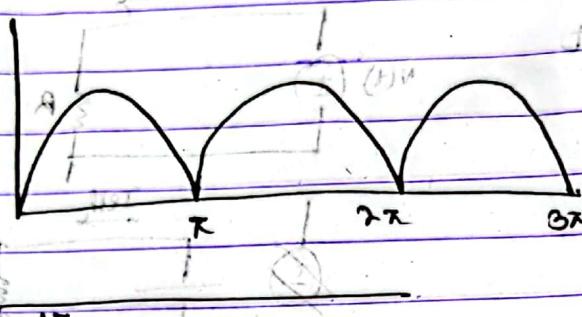

$$\text{Ans} \int_0^{\pi} (10 \sin^2 t)^2 dt = 0.0131$$

2018/08/09 2017/07/27/27

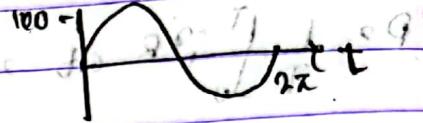

$$\begin{aligned} T &= 2\pi = \frac{1}{\omega} \quad \omega = 2\pi \\ v(t) &= 100 \sin(2\pi t + \phi) \\ &= 100 \sin(2\pi \frac{t}{T} + \phi) \\ &= 100 \sin t \end{aligned}$$

example 2: $\int_0^{\pi} (10 \sin^2 t)^2 dt = 0.0131$
Ans: 0.0131

$$C_1 + 200 \text{ mV} = 65 \text{ mV}$$

$$\frac{mV}{\mu V} = \frac{65}{200}$$

$$(200 - 65) \text{ mV} = 135 \text{ mV}$$

$$(200 - 65) \text{ mV} = \frac{135}{200} \text{ mV}$$

$$(200 - 65) \text{ mV} = 0.675 \text{ mV}$$